

myHDL Combinational Logic Elements: Demultiplexers (DEMUXs))

Steven K Armour

Table of Contents

- [1 Refrances](#)
- [2 Libraries and Helper functions](#)
- [3 Demultiplexers](#)
- [4 1 Channel Input: 2 Channel Output demultiplexer in Gate Level Logic](#)
 - [4.1 Sympy Expression](#)
 - [4.2 myHDL Module](#)
 - [4.3 myHDL Testing](#)
 - [4.4 Verilog Conversion](#)
 - [4.5 myHDL to Verilog Testbech](#)
 - [4.6 PYNQ-Z1 Deployment](#)
 - [4.6.1 Board Circuit](#)
 - [4.6.2 Board Constraints](#)
 - [4.6.3 Video of Deployment](#)
- [5 1 Channel Input:4 Channel Output demultiplexer in Gate Level Logic](#)
 - [5.1 Sympy Expression](#)
 - [5.2 myHDL Module](#)
 - [5.3 myHDL Testing](#)
 - [5.4 Verilog Conversion](#)
 - [5.5 myHDL to Verilog Testbench](#)
 - [5.6 PYNQ-Z1 Deployment](#)
 - [5.6.1 Board Circuit](#)
 - [5.6.2 Board Constraints](#)
 - [5.6.3 Video of Deployment](#)
- [6 1 Channel Input:4 Channel Output demultiplexer via DEMUX Stacking](#)
 - [6.1 myHDL Module](#)

▼ 1 Refrances

▼ 2 Libraries and Helper functions

```

In [1]: #This notebook also uses the `(some) LaTeX environments for Jupyter`
#https://github.com/ProfFan/latex_envs wich is part of the
#jupyter_contrib_nbextensions package

from myhdl import *
from myhdlpeek import Peeker
import numpy as np
import pandas as pd
import matplotlib.pyplot as plt
%matplotlib inline

from sympy import *
init_printing()

import itertools

#EE drawing tools in python from https://cdelker.bitbucket.io/SchemDraw
import SchemDraw as schem
import SchemDraw.elements as e
import SchemDraw.logic as l

#https://github.com/jrjohansson/version_information
%load_ext version_information
%version_information myhdl, myhdlpeek, numpy, pandas, matplotlib, sympy

```

```

Out[1]:

```

Software	Version
Python	3.6.2 64bit [GCC 4.4.7 20120313 (Red Hat 4.4.7-1)]
IPython	6.2.1
OS	Linux 4.15.0 30 generic x86_64 with debian stretch sid
myhdl	0.10
myhdlpeek	0.0.6
numpy	1.13.3
pandas	0.23.4
matplotlib	2.1.0
sympy	1.3
itertools	The 'itertools' distribution was not found and is required by the application
SchemDraw	0.3.0

Sun Sep 23 18:24:14 2018 MDT

```
In [2]: #helper functions to read in the .v and .vhd generated files into python
def VerilogTextReader(loc, printresult=True):
    with open(f'{loc}.v', 'r') as vText:
        VerilogText=vText.read()
    if printresult:
        print(f'***Verilog modual from {loc}.v***\n\n', VerilogText)
    return VerilogText

def VHDLTextReader(loc, printresult=True):
    with open(f'{loc}.vhd', 'r') as vText:
        VerilogText=vText.read()
    if printresult:
        print(f'***VHDL modual from {loc}.vhd***\n\n', VerilogText)
    return VerilogText

def ConstraintXDCTextReader(loc, printresult=True):
    with open(f'{loc}.xdc', 'r') as xdcText:
        ConstraintText=xdcText.read()
    if printresult:
        print(f'***Constraint file from {loc}.xdc***\n\n', ConstraintText)
    return ConstraintText
```

```
In [3]: def TruthTabelGenrator(BoolSymFunc):
    """
    Function to generate a truth table from a sympy boolean expression
    BoolSymFunc: sympy boolean expression
    return TT: a Truth table stored in a pandas dataframe
    """
    colsL=sorted([i for i in list(BoolSymFunc.rhs.atoms())], key=lambda x: x)
    colsR=sorted([i for i in list(BoolSymFunc.lhs.atoms())], key=lambda x: x)
    bitwidth=len(colsL)
    cols=colsL+colsR; cols

    TT=pd.DataFrame(columns=cols, index=range(2**bitwidth))

    for i in range(2**bitwidth):
        inputs=[int(j) for j in list(np.binary_repr(i, bitwidth))]
        outputs=BoolSymFunc.rhs.subs({j:v for j, v in zip(colsL, inputs)})
        inputs.append(int(bool(outputs)))
        TT.iloc[i]=inputs

    return TT
```

▼ 3 Demultiplexers

Definition 1 A Demultiplexer, typically referred to as a DEMUX, is a Digital(or analog) switching unit that takes one input channel to be streamed to a single output channel from many via a control input. For single input DEMUXs with 2^n outputs, there are then n input selection signals that make up the control word to select the output channel for the input.

Thus a DEMUX is the conjugate digital element to the MUX such that a MUX is an $N : 1$ mapping device and a DEMUX is a $1 : N$ mapping device.

From a behavioral standpoint DEMUXs are implemented with the same *if-elif-else* (*case*) control statements as a MUX but for each case, all outputs must be specified.

Furthermore, DEMUXs are often implemented via stacked MUXs since their governing equation is the Product SET (Cartesian product) all internal products of a MUXs SOP equation

▼ 4 1 Channel Input: 2 Channel Output demultiplexer in Gate Level Logic

 


Figure 1: 1:2 DEMUX Symbol and Gate internals

▼ 4.1 Sympy Expression

```
In [4]: x, s, y0, y1=symbols('x, s, y_0, y_1')
        y12_0Eq=Eq(y0, ~s&x)
        y12_1Eq=Eq(y1, s&x)
        y12_0Eq, y12_1Eq
```

Out[4]: $(y_0 = x \wedge \neg s, \quad y_1 = s \wedge x)$

```
In [5]: T0=TruthTabelGenrator(y12_0Eq)
        T1=TruthTabelGenrator(y12_1Eq)
        T10=pd.merge(T1, T0, how='left')
        T10
```

Out[5]:

	s	x	y_1	y_0
0	0	0	0	0
1	0	1	0	1
2	1	0	0	0
3	1	1	1	0

```
In [6]: y12_0EqN=lambdify([s, x], y12_0Eq.rhs, dummify=False)
        y12_1EqN=lambdify([s, x], y12_1Eq.rhs, dummify=False)
        SystmaticVals=np.array(list(itertools.product([0,1], repeat=2)))
        print(SystmaticVals)
        print(y12_0EqN(SystmaticVals[:, 0], SystmaticVals[:, 1]).astype(int))
        print(y12_1EqN(SystmaticVals[:, 0], SystmaticVals[:, 1]).astype(int))
```

```
[[0 0]
 [0 1]
 [1 0]
 [1 1]]
[0 1 0 0]
[0 0 0 1]
```

▼ 4.2 myHDL Module

```
In [7]: @block
def DEMUX1_2_Combo(x, s, y0, y1):
    """
    1:2 DEMUX written in full combo
    Inputs:
        x(bool): input feed
        s(bool): channel select
    Outputs:
        y0(bool): ouput channel 0
        y1(bool): ouput channel 1
    """

    @always_comb
    def logic():
        y0.next= not s and x
        y1.next= s and x

    return instances()
```

▼ 4.3 myHDL Testing

```
In [8]: TestLen=10
        SystmaticVals=list(itertools.product([0,1], repeat=2))

        xTVs=np.array([i[1] for i in SystmaticVals]).astype(int)
        np.random.seed(15)
        xTVs=np.append(xTVs, np.random.randint(0,2, TestLen)).astype(int)

        sTVs=np.array([i[0] for i in SystmaticVals]).astype(int)
        #the random genrator must have a differint seed between each generation
        #call in order to produce differint values for each call
        np.random.seed(16)
        sTVs=np.append(sTVs, np.random.randint(0,2, TestLen)).astype(int)

        TestLen=len(xTVs)
        SystmaticVals, sTVs, xTVs
```

```
Out[8]: ((0, 0), (0, 1), (1, 0), (1, 1)),
        array([0, 0, 1, 1, 1, 0, 1, 1, 1, 1, 0, 1, 1, 0]),
        array([0, 1, 0, 1, 0, 1, 0, 1, 1, 0, 0, 1, 1, 1]))
```

```

In [9]: Peeker.clear()
x=Signal(bool(0)); Peeker(x, 'x')
s=Signal(bool(0)); Peeker(s, 's')
y0=Signal(bool(0)); Peeker(y0, 'y0')
y1=Signal(bool(0)); Peeker(y1, 'y1')

DUT=DEMUX1_2_Combo(x, s, y0, y1)

▼ def DEMUX1_2_Combo_TB():
    """
    myHDL only testbench for module `DEMUX1_2_Combo`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            x.next=int(xTVs[i])
            s.next=int(sTVs[i])

            yield delay(1)

            raise StopSimulation()

        return instances()


sim=Simulation(DUT, DEMUX1_2_Combo_TB(), *Peeker.instances()).run()

```

```

In [10]: Peeker.to_wavedrom('x', 's', 'y0','y1')

```

 

```
In [11]: DEMUX1_2_ComboData=Peeker.to_dataframe()
DEMUX1_2_ComboData=DEMUX1_2_ComboData[['x', 's', 'y0','y1']]
DEMUX1_2_ComboData
```

Out[11]:

	x	s	y0	y1
0	0	0	0	0
1	1	0	1	0
2	0	1	0	0
3	1	1	0	1
4	0	1	0	0
5	1	0	1	0
6	0	1	0	0
7	1	1	0	1
9	0	1	0	0
10	0	0	0	0
11	1	1	0	1
13	1	0	1	0

```
In [12]: DEMUX1_2_ComboData['y0Ref']=DEMUX1_2_ComboData.apply(lambda row:y12_0Ec
DEMUX1_2_ComboData['y1Ref']=DEMUX1_2_ComboData.apply(lambda row:y12_1Ec
DEMUX1_2_ComboData
```

Out[12]:

	x	s	y0	y1	y0Ref	y1Ref
0	0	0	0	0	0	0
1	1	0	1	0	1	0
2	0	1	0	0	0	0
3	1	1	0	1	0	1
4	0	1	0	0	0	0
5	1	0	1	0	1	0
6	0	1	0	0	0	0
7	1	1	0	1	0	1
9	0	1	0	0	0	0
10	0	0	0	0	0	0
11	1	1	0	1	0	1
13	1	0	1	0	1	0


```
In [13]: Test0=(DEMUX1_2_ComboData['y0']==DEMUX1_2_ComboData['y0Ref']).all()
Test1=(DEMUX1_2_ComboData['y1']==DEMUX1_2_ComboData['y1Ref']).all()
Test=Test0&Test1
print(f'Module `DEMUX1_2_Combo` works as expected: {Test}')
```

Module `DEMUX1_2_Combo` works as expected: True

▼ 4.4 Verilog Conversion

```
In [14]: DUT.convert()
VerilogTextReader('DEMUX1_2_Combo');
```

Verilog modular from DEMUX1_2_Combo.v

```
// File: DEMUX1_2_Combo.v
// Generated by MyHDL 0.10
// Date: Sun Sep 23 18:24:15 2018
```

```
`timescale 1ns/10ps
```

```
module DEMUX1_2_Combo (
    x,
    s,
    y0,
    y1
);
// 1:2 DEMUX written in full combo
// Inputs:
//     x(bool): input feed
//     s(bool): channel select
// Outputs:
//     y0(bool): ouput channel 0
//     y1(bool): ouput channel 1
```

```
input x;
input s;
output y0;
wire y0;
output y1;
wire y1;
```

```
assign y0 = ((!s) && x);
assign y1 = (s && x);
```

```
endmodule
```

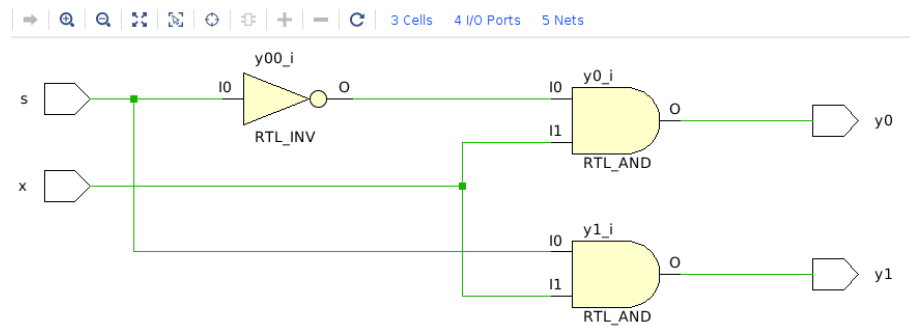


Figure 2: DEMUX1_2_Combo RTL schematic; Xilinx Vivado 2017.4

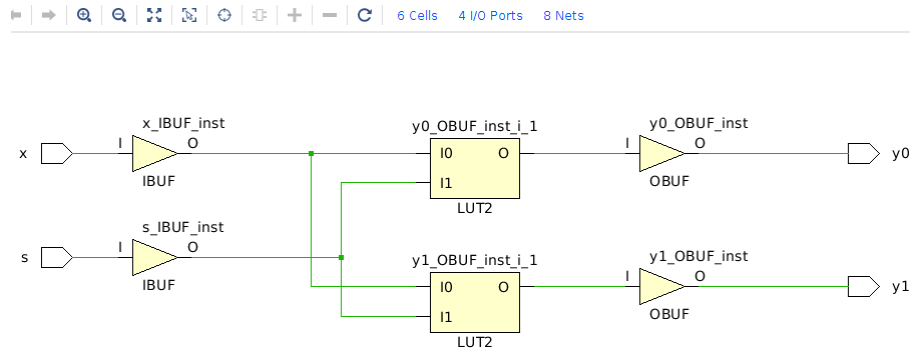


Figure 3: DEMUX1_2_Combo Synthesized Schematic; Xilinx Vivado 2017.4

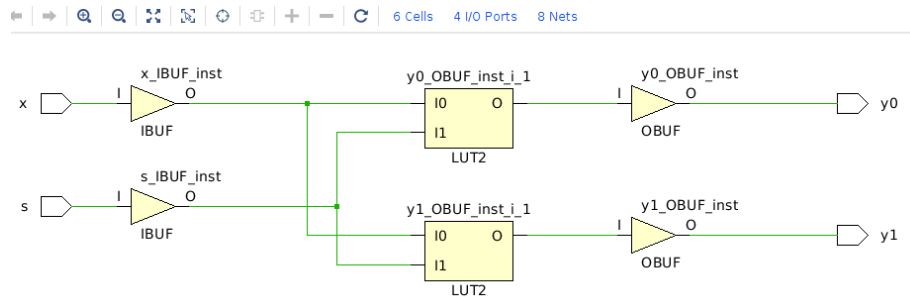


Figure 4: DEMUX1_2_Combo Implemented Schematic; Xilinx Vivado 2017.4

▼ 4.5 myHDL to Verilog Testbech

```
In [15]: ▼ #create BitVectors
xTVs=intbv(int(''.join(xTVs.astype(str)), 2))[TestLen:]
sTVs=intbv(int(''.join(sTVs.astype(str)), 2))[TestLen:]

xTVs, bin(xTVs), sTVs, bin(sTVs)
```

```
Out[15]: (intbv(5479), '1010101100111', intbv(3830), '111011110110')
```

```

In [16]: @block
def DEMUX1_2_Combo_TBV():
    """
    myHDL -> testbench for module `DEMUX1_2_Combo`
    """

    x=Signal(bool(0))
    s=Signal(bool(0))
    y0=Signal(bool(0))
    y1=Signal(bool(0))

    @always_comb
    def print_data():
        print(x, s, y0, y1)

    #Test Signal Bit Vectors

    xTV=Signal(xTVs)
    sTV=Signal(sTVs)

    DUT=DEMUX1_2_Combo(x, s, y0, y1)

    @instance
    def stimules():
        for i in range(TestLen):
            x.next=int(xTV[i])
            s.next=int(sTV[i])

            yield delay(1)

        raise StopSimulation()

    return instances()

TB=DEMUX1_2_Combo_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('DEMUX1_2_Combo_TBV');

```

```

<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from DEMUX1_2_Combo_TBV.v***

```

```

// File: DEMUX1_2_Combo_TBV.v
// Generated by MyHDL 0.10
// Date: Sun Sep 23 18:24:16 2018

```

```

`timescale 1ns/10ps

```

```

module DEMUX1_2_Combo_TBV (

```

```

);
// myHDL -> testbench for module `DEMUX1_2_Combo`

```

```

reg x = 0;
reg s = 0;
wire y0;
wire y1;
wire [13:0] xTV;
wire [13:0] sTV;

assign xTV = 14'd5479;
assign sTV = 14'd3830;

always @(x, y0, s, y1) begin: DEMUX1_2_COMBO_TBV_PRINT_DATA
    $write("%h", x);
    $write(" ");
    $write("%h", s);
    $write(" ");
    $write("%h", y0);
    $write(" ");
    $write("%h", y1);
    $write("\n");
end

assign y0 = ((!s) && x);
assign y1 = (s && x);

initial begin: DEMUX1_2_COMBO_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        x <= xTV[i];
        s <= sTV[i];
        # 1;
    end
    $finish;
end

endmodule

```

```

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: xTV
    category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: sTV
    category=ToVerilogWarning

```

▼ 4.6 PYNQ-Z1 Deployment

▼ 4.6.1 Board Circuit

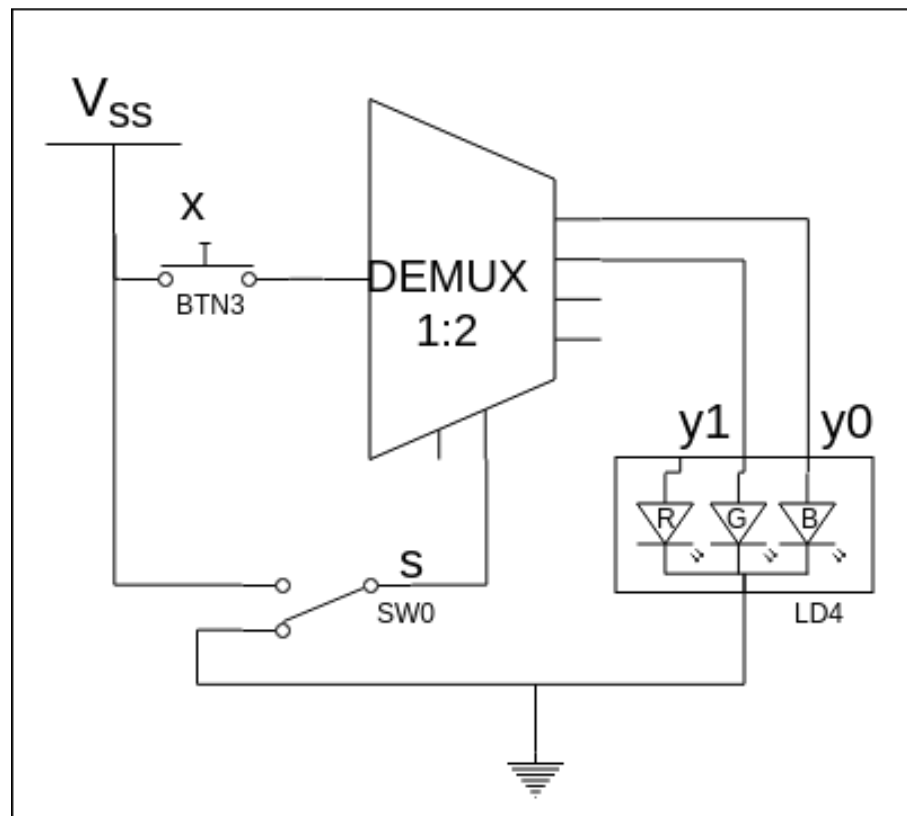


Figure 5: 1:2 DEMUX PYNQ-Z1 (Non SoC) conceptualized circuit

▼ 4.6.2 Board Constraints

```
In [17]: ConstraintXDCTextReader('DEMUX1_2');

***Constraint file from DEMUX1_2.xdc***

## Switches
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports
{s}]; ##SW0

## Buttons
set_property -dict {PACKAGE_PIN L19 IOSTANDARD LVCMOS33} [get_ports
{x}]; ##BT3

## RGBLEDs
set_property -dict { PACKAGE_PIN L15    IOSTANDARD LVCMOS33 } [get_ports
{y0}]; ##LD4_Blue
set_property -dict { PACKAGE_PIN G17    IOSTANDARD LVCMOS33 } [get_ports
{y1}]; ##LD4_Green
```

▼ 4.6.3 Video of Deployment

DEMUX1_2_Combo on PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=LJG4Z2kxEKE\)](https://www.youtube.com/watch?v=LJG4Z2kxEKE))

▼ 5 1 Channel Input:4 Channel Output demultiplexer in Gate Level Logic

▼ 5.1 Sympy Expression

```
In [18]: x, s0, s1, y0, y1, y2, y3=symbols('x, s0, s1, y0, y1, y2, y3')
y14_0Eq=Eq(y0, ~s0&~s1&x)
y14_1Eq=Eq(y1, s0&~s1&x)
y14_2Eq=Eq(y2, ~s0&s1&x)
y14_3Eq=Eq(y3, s0&s1&x)
y14_0Eq, y14_1Eq, y14_2Eq, y14_3Eq
```

Out[18]: $(y_0 = x \wedge \neg s_0 \wedge \neg s_1, \quad y_1 = s_0 \wedge x \wedge \neg s_1, \quad y_2 = s_1 \wedge x \wedge \neg s_0, \quad y_3 = s_0 \wedge s_1 \wedge x)$

```
In [19]: T0=TruthTabelGenrator(y14_0Eq)
T1=TruthTabelGenrator(y14_1Eq)
T2=TruthTabelGenrator(y14_2Eq)
T3=TruthTabelGenrator(y14_3Eq)
T10=pd.merge(T1, T0, how='left')
T20=pd.merge(T2, T10, how='left')
T30=pd.merge(T3, T20, how='left')
T30
```

Out[19]:

	s0	s1	x	y3	y2	y1	y0
0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	1
2	0	1	0	0	0	0	0
3	0	1	1	0	1	0	0
4	1	0	0	0	0	0	0
5	1	0	1	0	0	1	0
6	1	1	0	0	0	0	0
7	1	1	1	1	0	0	0

```
In [20]: y14_0EqN=lambdify([x, s0, s1], y14_0Eq.rhs, dummify=False)
y14_1EqN=lambdify([x, s0, s1], y14_1Eq.rhs, dummify=False)
y14_2EqN=lambdify([x, s0, s1], y14_2Eq.rhs, dummify=False)
y14_3EqN=lambdify([x, s0, s1], y14_3Eq.rhs, dummify=False)
SystmaticVals=np.array(list(itertools.product([0,1], repeat=3)))
print(SystmaticVals)
print(y14_0EqN(SystmaticVals[:, 2], SystmaticVals[:, 1], SystmaticVals[:, 0]))
print(y14_1EqN(SystmaticVals[:, 2], SystmaticVals[:, 1], SystmaticVals[:, 0]))
print(y14_2EqN(SystmaticVals[:, 2], SystmaticVals[:, 1], SystmaticVals[:, 0]))
print(y14_3EqN(SystmaticVals[:, 2], SystmaticVals[:, 1], SystmaticVals[:, 0]))
```

```
[[0 0 0]
 [0 0 1]
 [0 1 0]
 [0 1 1]
 [1 0 0]
 [1 0 1]
 [1 1 0]
 [1 1 1]]
[[0 1 0 0 0 0 0 0]
 [0 0 0 1 0 0 0 0]
 [0 0 0 0 0 1 0 0]
 [0 0 0 0 0 0 0 1]]
```

▼ 5.2 myHDL Module

```
In [21]: @block
▼ def DEMUX1_4_Combo(x, s0, s1, y0, y1, y2, y3):
    """
    1:4 DEMUX written in full combo

    Inputs:
        x(bool): input feed
        s0(bool): channel select 0
        s1(bool): channel select 1

    Outputs:
        y0(bool): ouput channel 0
        y1(bool): ouput channel 1
        y2(bool): ouput channel 2
        y3(bool): ouput channel 3
    """

    @always_comb
    ▼ def logic():
        y0.next= (not s0) and (not s1) and x
        y1.next= s0 and (not s1) and x
        y2.next= (not s0) and s1 and x
        y3.next= s0 and s1 and x

    return instances()
```

▼ 5.3 myHDL Testing

```
In [22]: TestLen=10
         SystmaticVals=list(itertools.product([0,1], repeat=3))

         xTVs=np.array([i[2] for i in SystmaticVals]).astype(int)
         np.random.seed(15)
         xTVs=np.append(xTVs, np.random.randint(0,2, TestLen)).astype(int)

         s0TVs=np.array([i[1] for i in SystmaticVals]).astype(int)
         #the random genrator must have a differint seed beween each generation
         #call in order to produce differint values for each call
         np.random.seed(16)
         s0TVs=np.append(s0TVs, np.random.randint(0,2, TestLen)).astype(int)

         s1TVs=np.array([i[0] for i in SystmaticVals]).astype(int)
         #the random genrator must have a differint seed beween each generation
         #call in order to produce differint values for each call
         np.random.seed(17)
         s1TVs=np.append(s1TVs, np.random.randint(0,2, TestLen)).astype(int)

         TestLen=len(xTVs)
         SystmaticVals, xTVs, s0TVs, s1TVs
```

```
Out[22]: ([ (0, 0, 0),
             (0, 0, 1),
             (0, 1, 0),
             (0, 1, 1),
             (1, 0, 0),
             (1, 0, 1),
             (1, 1, 0),
             (1, 1, 1)],
          array([0, 1, 0, 1, 0, 1, 0, 1, 0, 1, 0, 1, 1, 0, 0, 1, 1, 1]),
          array([0, 0, 1, 1, 0, 0, 1, 1, 1, 0, 1, 1, 1, 1, 0, 1, 1, 0]),
          array([0, 0, 0, 0, 1, 1, 1, 1, 1, 1, 1, 0, 0, 1, 0, 1, 0, 1]))
```


In [23]:

```
Peeker.clear()
x=Signal(bool(0)); Peeker(x, 'x')
s0=Signal(bool(0)); Peeker(s0, 's0')
s1=Signal(bool(0)); Peeker(s1, 's1')
y0=Signal(bool(0)); Peeker(y0, 'y0')
y1=Signal(bool(0)); Peeker(y1, 'y1')
y2=Signal(bool(0)); Peeker(y2, 'y2')
y3=Signal(bool(0)); Peeker(y3, 'y3')

DUT=DEMUX1_4_Combo(x, s0, s1, y0, y1, y2, y3)

▼ def DEMUX1_4_Combo_TB():
    """
    myHDL only testbench for module `DEMUX1_4_Combo`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            x.next=int(xTVs[i])
            s0.next=int(s0TVs[i])
            s1.next=int(s1TVs[i])

            yield delay(1)


            raise StopSimulation()

        return instances()

sim=Simulation(DUT, DEMUX1_4_Combo_TB(), *Peeker.instances()).run()
```

In [24]:
 
```
Peeker.to_wavedrom('x', 's1', 's0', 'y0', 'y1', 'y2', 'y3')
```



```
In [25]: DEMUX1_4_ComboData=Peeker.to_dataframe()  
DEMUX1_4_ComboData=DEMUX1_4_ComboData[['x', 's1', 's0', 'y0', 'y1', 'y2', 'y3']]  
DEMUX1_4_ComboData
```

Out[25]:

	x	s1	s0	y0	y1	y2	y3
0	0	0	0	0	0	0	0
1	1	0	0	1	0	0	0
2	0	0	1	0	0	0	0
3	1	0	1	0	1	0	0
4	0	1	0	0	0	0	0
5	1	1	0	0	0	1	0
6	0	1	1	0	0	0	0
7	1	1	1	0	0	0	1
8	0	1	1	0	0	0	0
9	1	1	0	0	0	1	0
10	0	1	1	0	0	0	0
11	1	0	1	0	1	0	0
13	0	1	1	0	0	0	0
14	0	0	0	0	0	0	0
15	1	1	1	0	0	0	1
16	1	0	1	0	1	0	0
17	1	1	0	0	0	1	0

```
In [26]: DEMUX1_4_ComboData['y0Ref']=DEMUX1_4_ComboData.apply(lambda row:y14_0Ec
DEMUX1_4_ComboData['y1Ref']=DEMUX1_4_ComboData.apply(lambda row:y14_1Ec
DEMUX1_4_ComboData['y2Ref']=DEMUX1_4_ComboData.apply(lambda row:y14_2Ec
DEMUX1_4_ComboData['y3Ref']=DEMUX1_4_ComboData.apply(lambda row:y14_3Ec
DEMUX1_4_ComboData
```

Out[26]:

	x	s1	s0	y0	y1	y2	y3	y0Ref	y1Ref	y2Ref	y3Ref
0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	1	0	0	0	1	0	0	0
2	0	0	1	0	0	0	0	0	0	0	0
3	1	0	1	0	1	0	0	0	1	0	0
4	0	1	0	0	0	0	0	0	0	0	0
5	1	1	0	0	0	1	0	0	0	1	0
6	0	1	1	0	0	0	0	0	0	0	0
7	1	1	1	0	0	0	1	0	0	0	1
8	0	1	1	0	0	0	0	0	0	0	0
9	1	1	0	0	0	1	0	0	0	1	0
10	0	1	1	0	0	0	0	0	0	0	0
11	1	0	1	0	1	0	0	0	1	0	0
13	0	1	1	0	0	0	0	0	0	0	0
14	0	0	0	0	0	0	0	0	0	0	0
15	1	1	1	0	0	0	1	0	0	0	1
16	1	0	1	0	1	0	0	0	1	0	0
17	1	1	0	0	0	1	0	0	0	1	0

```
In [27]: Test0=(DEMUX1_4_ComboData['y0']==DEMUX1_4_ComboData['y0Ref']).all()
Test1=(DEMUX1_4_ComboData['y1']==DEMUX1_4_ComboData['y1Ref']).all()
Test2=(DEMUX1_4_ComboData['y2']==DEMUX1_4_ComboData['y2Ref']).all()
Test3=(DEMUX1_4_ComboData['y3']==DEMUX1_4_ComboData['y3Ref']).all()
Test=Test0&Test1&Test2&Test3
print(f'Module `DEMUX1_4_Combo` works as exspected: {Test}')
```

Module `DEMUX1_4_Combo` works as exspected: True

▼ 5.4 Verilog Conversion

In [28]:

```
DUT.convert()  
VerilogTextReader('DEMUX1_4_Combo');
```

```
***Verilog modular from DEMUX1_4_Combo.v***
```

```
// File: DEMUX1_4_Combo.v  
// Generated by MyHDL 0.10  
// Date: Sun Sep 23 18:24:17 2018
```

```
`timescale 1ns/10ps
```

```
module DEMUX1_4_Combo (  
    x,  
    s0,  
    s1,  
    y0,  
    y1,  
    y2,  
    y3  
);  
// 1:4 DEMUX written in full combo  
//  
// Inputs:  
//     x(bool): input feed  
//     s0(bool): channel select 0  
//     s1(bool): channel select 1  
//  
// Outputs:  
//     y0(bool): ouput channel 0  
//     y1(bool): ouput channel 1  
//     y2(bool): ouput channel 2  
//     y3(bool): ouput channel 3
```

```
input x;  
input s0;  
input s1;  
output y0;  
wire y0;  
output y1;  
wire y1;  
output y2;  
wire y2;  
output y3;  
wire y3;
```

```
assign y0 = ((!s0) && (!s1) && x);  
assign y1 = (s0 && (!s1) && x);  
assign y2 = ((!s0) && s1 && x);  
assign y3 = (s0 && s1 && x);
```

```
endmodule
```

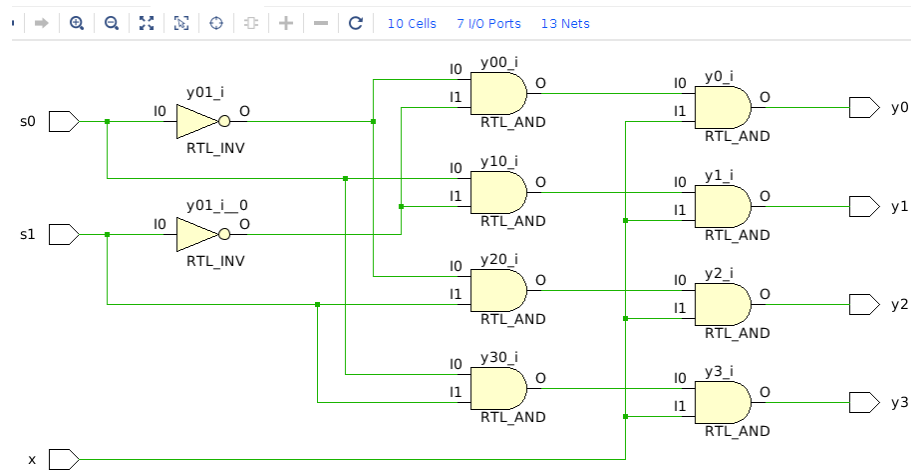


Figure 6: DEMUX1_4_Combo RTL schematic; Xilinx Vivado 2017.4

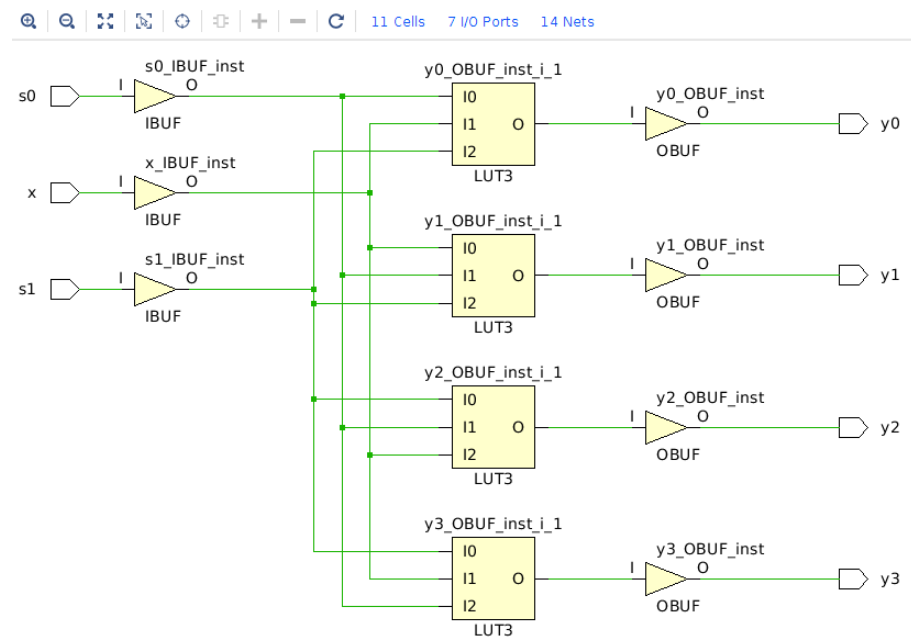


Figure 7: DEMUX1_4_Combo Synthesized Schematic; Xilinx Vivado 2017.4

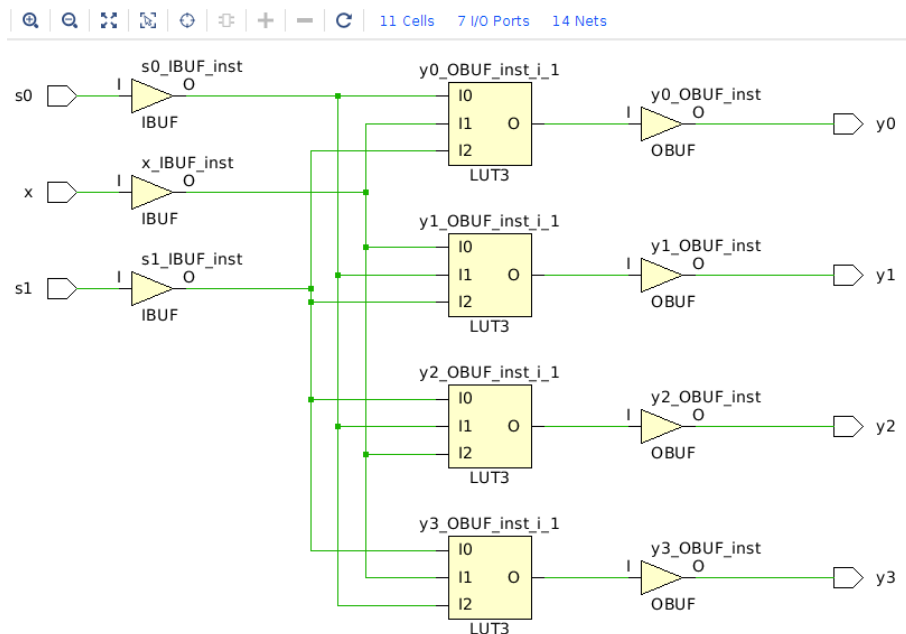


Figure 8: DEMUX1_4_Combo Implemented Schematic; Xilinx Vivado 2017.4

▼ 5.5 myHDL to Verilog Testbench

```
In [29]: ▼ #create BitVectors
xTVs=intbv(int(''.join(xTVs.astype(str)), 2))[TestLen:]
s0TVs=intbv(int(''.join(s0TVs.astype(str)), 2))[TestLen:]
s1TVs=intbv(int(''.join(s1TVs.astype(str)), 2))[TestLen:]

xTVs, bin(xTVs), s0TVs, bin(s0TVs), s1TVs, bin(s1TVs)
```

```
Out[29]: (intbv(87399),
'10101010101100111',
intbv(52982),
'1100111011110110',
intbv(16277),
'11111110010101')
```

```

In [30]: @block
          ▼ def DEMUX1_4_Combo_TBV():
              """
              myHDL -> testbench for module `DEMUX1_4_Combo`
              """

              x=Signal(bool(0))
              s0=Signal(bool(0))
              s1=Signal(bool(0))
              y0=Signal(bool(0))
              y1=Signal(bool(0))
              y2=Signal(bool(0))
              y3=Signal(bool(0))

              @always_comb
              ▼ def print_data():
                  print(x, s0, s1, y0, y1, y2, y3)

              #Test Signal Bit Vectors

              xTV=Signal(xTVs)
              s0TV=Signal(s0TVs)
              s1TV=Signal(s1TVs)

              DUT=DEMUX1_4_Combo(x, s0, s1, y0, y1, y2, y3)

              @instance
              ▼ def stimules():
                  ▼ for i in range(TestLen):
                      x.next=int(xTV[i])
                      s0.next=int(s0TV[i])
                      s1.next=int(s1TV[i])

                      yield delay(1)

                      raise StopSimulation()

              return instances()

              TB=DEMUX1_4_Combo_TBV()
              TB.convert(hdl="Verilog", initial_values=True)
              VerilogTextReader('DEMUX1_4_Combo_TBV');

```

```

<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from DEMUX1_4_Combo_TBV.v***

```

```

// File: DEMUX1_4_Combo_TBV.v
// Generated by MyHDL 0.10
// Date: Sun Sep 23 18:24:18 2018

```

```

`timescale 1ns/10ps

module DEMUX1_4_Combo_TBV (

);
// myHDL -> testbench for module `DEMUX1_4_Combo`

reg x = 0;
wire y0;
wire y1;
reg s0 = 0;
reg s1 = 0;
wire y2;
wire y3;
wire [17:0] xTV;
wire [17:0] s0TV;
wire [17:0] s1TV;

assign xTV = 18'd87399;
assign s0TV = 18'd52982;
assign s1TV = 18'd16277;

always @(x, y0, s1, s0, y3, y2, y1) begin: DEMUX1_4_COMBO_TBV_PRINT_DATA
    $write("%h", x);
    $write(" ");
    $write("%h", s0);
    $write(" ");
    $write("%h", s1);
    $write(" ");
    $write("%h", y0);
    $write(" ");
    $write("%h", y1);
    $write(" ");
    $write("%h", y2);
    $write(" ");
    $write("%h", y3);
    $write("\n");
end

assign y0 = ((!s0) && (!s1) && x);
assign y1 = (s0 && (!s1) && x);
assign y2 = ((!s0) && s1 && x);
assign y3 = (s0 && s1 && x);

initial begin: DEMUX1_4_COMBO_TBV_STIMULES
    integer i;
    for (i=0; i<18; i=i+1) begin
        x <= xTV[i];
        s0 <= s0TV[i];
    end
end

```



```

        s1 <= s1TV[i];
        # 1;
    end
    $finish;
end

endmodule

```

```

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: xTV
    category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: s0TV
    category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: s1TV
    category=ToVerilogWarning

```

▼ 5.6 PYNQ-Z1 Deployment

▼ 5.6.1 Board Circuit

 


Figure 9: 1:4 DEMUX PYNQ-Z1 (Non SoC) conceptualized circuit

▼ 5.6.2 Board Constraints

In [31]: `ConstraintXDCTextReader('DEMUX1_4');`

```
***Constraint file from DEMUX1_4.xdc***
```

```
## Switches
```

```
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {s0}]; ##SW0
```

```
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {s1}]; ##SW1
```

```
## Buttons
```

```
set_property -dict {PACKAGE_PIN L19 IOSTANDARD LVCMOS33} [get_ports {x}]; ##BT3
```

```
## RGBLEDs
```

```
set_property -dict { PACKAGE_PIN L15 IOSTANDARD LVCMOS33 } [get_ports {y0}]; ##LD4_Blue
```

```
set_property -dict { PACKAGE_PIN G17 IOSTANDARD LVCMOS33 } [get_ports {y1}]; ##LD4_Green
```

```
set_property -dict { PACKAGE_PIN L14 IOSTANDARD LVCMOS33 } [get_ports {y2}]; ##LD5_Green
```

```
set_property -dict { PACKAGE_PIN M15 IOSTANDARD LVCMOS33 } [get_ports {y3}]; ##LD5_Red
```

▼ 5.6.3 Video of Deployment

DEMUX1_4_Combo on PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=VT5lly8dMdg\)](https://www.youtube.com/watch?v=VT5lly8dMdg))

▼ 6 1 Channel Input:4 Channel Output demultiplexer via DEMUX Stacking

▼ 6.1 myHDL Module

```

In [32]: @block
▼ def DEMUX1_4_DMS(x, s0, s1, y0, y1, y2, y3):
    """
    1:4 DEMUX via DEMUX Stacking
    Inputs:
        x(bool): input feed
        s0(bool): channel select 0
        s1(bool): channel select 1
    Outputs:
        y0(bool): ouput channel 0
        y1(bool): ouput channel 1
        y2(bool): ouput channel 2
        y3(bool): ouput channel 3
    """

    s0_y0y1_WIRE=Signal(bool(0))
    s0_y2y3_WIRE=Signal(bool(0))
    x_s1_DEMUX=DEMUX1_2_Combo(x, s1, s0_y0y1_WIRE, s0_y2y3_WIRE)

    s1_y0y1_DEMUX=DEMUX1_2_Combo(s0_y0y1_WIRE, s0, y0, y1)
    s1_y2y3_DEMUX=DEMUX1_2_Combo(s0_y2y3_WIRE, s0, y2, y3)

    return instances()

```

▼ 6.2 myHDL Testing

In [33]:

```
TestLen=10
SystmaticVals=list(itertools.product([0,1], repeat=3))

xTVs=np.array([i[2] for i in SystmaticVals]).astype(int)
np.random.seed(15)
xTVs=np.append(xTVs, np.random.randint(0,2, TestLen)).astype(int)

s0TVs=np.array([i[1] for i in SystmaticVals]).astype(int)
#the random genrator must have a differint seed beween each generation
#call in order to produce differint values for each call
np.random.seed(16)
s0TVs=np.append(s0TVs, np.random.randint(0,2, TestLen)).astype(int)

s1TVs=np.array([i[0] for i in SystmaticVals]).astype(int)
#the random genrator must have a differint seed beween each generation
#call in order to produce differint values for each call
np.random.seed(17)
s1TVs=np.append(s1TVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(xTVs)
SystmaticVals, xTVs, s0TVs, s1TVs
```

Out[33]:

```
((0, 0, 0),
 (0, 0, 1),
 (0, 1, 0),
 (0, 1, 1),
 (1, 0, 0),
 (1, 0, 1),
 (1, 1, 0),
 (1, 1, 1)),
array([0, 1, 0, 1, 0, 1, 0, 1, 0, 1, 0, 1, 1, 0, 0, 1, 1, 1]),
array([0, 0, 1, 1, 0, 0, 1, 1, 1, 0, 1, 1, 1, 1, 0, 1, 1, 0]),
array([0, 0, 0, 0, 1, 1, 1, 1, 1, 1, 1, 0, 0, 1, 0, 1, 0, 1]))
```

In [34]:

```
Peeker.clear()
x=Signal(bool(0)); Peeker(x, 'x')
s0=Signal(bool(0)); Peeker(s0, 's0')
s1=Signal(bool(0)); Peeker(s1, 's1')
y0=Signal(bool(0)); Peeker(y0, 'y0')
y1=Signal(bool(0)); Peeker(y1, 'y1')
y2=Signal(bool(0)); Peeker(y2, 'y2')
y3=Signal(bool(0)); Peeker(y3, 'y3')

DUT=DEMUX1_4_DMS(x, s0, s1, y0, y1, y2, y3)

▼ def DEMUX1_4_DMS_TB():
    """
    myHDL only testbench for module `DEMUX1_4_DMS`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            x.next=int(xTVs[i])
            s0.next=int(s0TVs[i])
            s1.next=int(s1TVs[i])

            yield delay(1)


            raise StopSimulation()

        return instances()

sim=Simulation(DUT, DEMUX1_4_DMS_TB(), *Peeker.instances()).run()
```

In [35]:
 
```
Peeker.to_wavedrom('x', 's1', 's0', 'y0', 'y1', 'y2', 'y3')
```



```
In [36]: DEMUX1_4_DMSData=Peeker.to_dataframe()
DEMUX1_4_DMSData=DEMUX1_4_DMSData[['x', 's1', 's0', 'y0', 'y1', 'y2', 'y3']]
DEMUX1_4_DMSData
```

Out[36]:

	x	s1	s0	y0	y1	y2	y3
0	0	0	0	0	0	0	0
1	1	0	0	1	0	0	0
2	0	0	1	0	0	0	0
3	1	0	1	0	1	0	0
4	0	1	0	0	0	0	0
5	1	1	0	0	0	1	0
6	0	1	1	0	0	0	0
7	1	1	1	0	0	0	1
8	0	1	1	0	0	0	0
9	1	1	0	0	0	1	0
10	0	1	1	0	0	0	0
11	1	0	1	0	1	0	0
13	0	1	1	0	0	0	0
14	0	0	0	0	0	0	0
15	1	1	1	0	0	0	1
16	1	0	1	0	1	0	0
17	1	1	0	0	0	1	0

```
In [37]: Test=DEMUX1_4_DMSData==DEMUX1_4_ComboData[['x', 's1', 's0', 'y0', 'y1', 'y2', 'y3']]
Test=Test.all().all()
print(f'DEMUX1_4_DMS equivlinet to DEMUX1_4_Combo: {Test}')
```

DEMUX1_4_DMS equivlinet to DEMUX1_4_Combo: True

▼ 6.3 Verilog Conversion

In [38]:

```
DUT.convert()
VerilogTextReader('DEMUX1_4_DMS');

***Verilog modular from DEMUX1_4_DMS.v***

// File: DEMUX1_4_DMS.v
// Generated by MyHDL 0.10
// Date: Sun Sep 23 18:24:20 2018

`timescale 1ns/10ps

module DEMUX1_4_DMS (
    x,
    s0,
    s1,
    y0,
    y1,
    y2,
    y3
);
// 1:4 DEMUX via DEMUX Stacking
// Inputs:
//     x(bool): input feed
//     s0(bool): channel select 0
//     s1(bool): channel select 1
//
// Outputs:
//     y0(bool): ouput channel 0
//     y1(bool): ouput channel 1
//     y2(bool): ouput channel 2
//     y3(bool): ouput channel 3

input x;
input s0;
input s1;
output y0;
wire y0;
output y1;
wire y1;
output y2;
wire y2;
output y3;
wire y3;

wire s0_y2y3_WIRE;
wire s0_y0y1_WIRE;

assign s0_y0y1_WIRE = ((!s1) && x);
assign s0_y2y3_WIRE = (s1 && x);

assign y0 = ((!s0) && s0_y0y1_WIRE);
```

```
assign y1 = (s0 && s0_y0y1_WIRE);
```

```
assign y2 = ((!s0) && s0_y2y3_WIRE);  
assign y3 = (s0 && s0_y2y3_WIRE);
```

```
endmodule
```

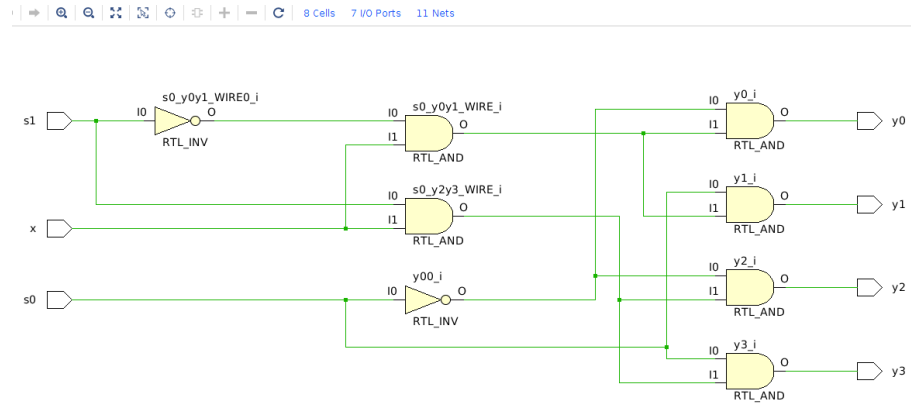


Figure 10: DEMUX1_4_DMS RTL schematic; Xilinx Vivado 2017.4

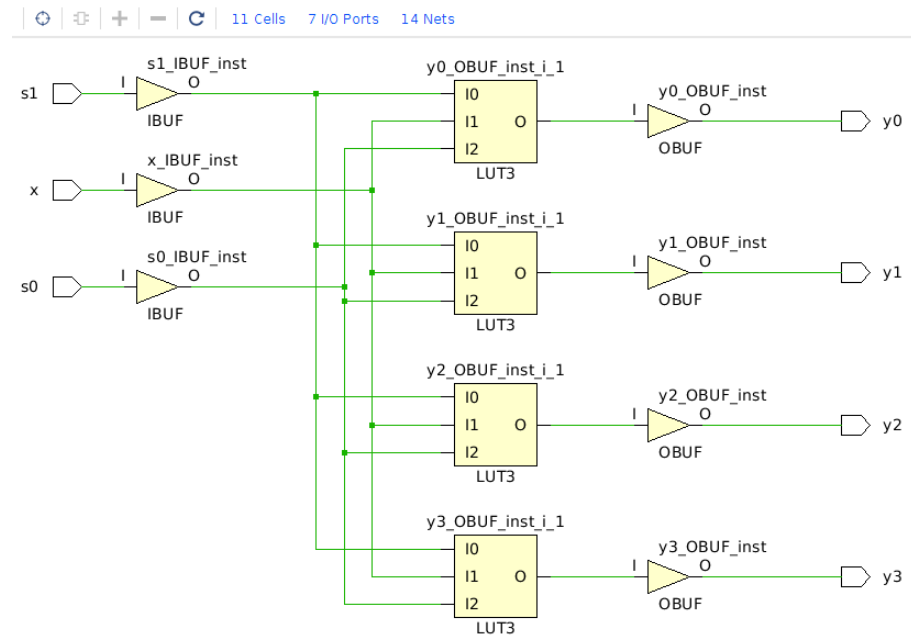


Figure 11: DEMUX1_4_DMS Synthesized Schematic; Xilinx Vivado 2017.4

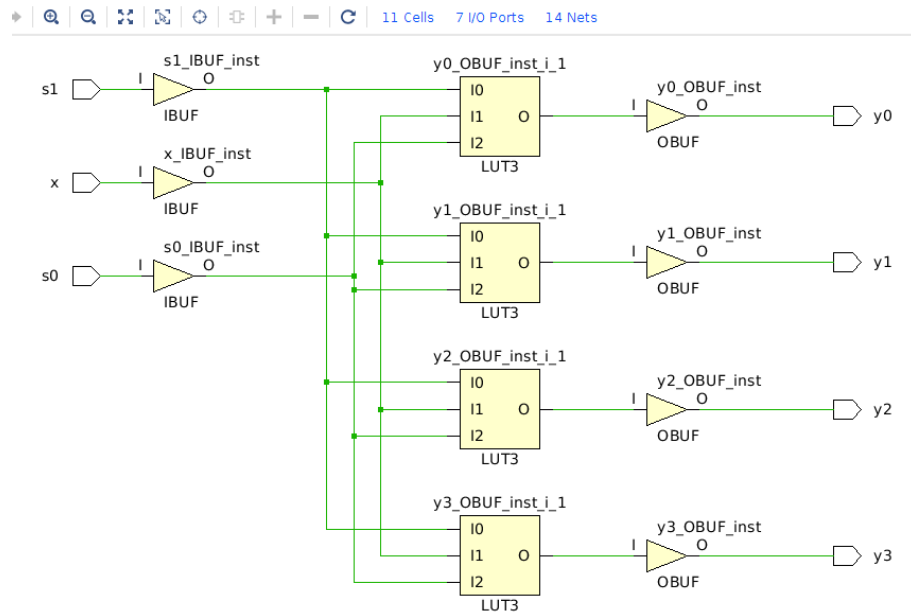


Figure 12: DEMUX1_4_DMS Implemented Schematic; Xilinx Vivado 2017.4

▼ 6.4 myHDL to Verilog Testbench

```
In [39]: ▼ #create BitVectors
xTVs=intbv(int(''.join(xTVs.astype(str)), 2))[TestLen:]
s0TVs=intbv(int(''.join(s0TVs.astype(str)), 2))[TestLen:]
s1TVs=intbv(int(''.join(s1TVs.astype(str)), 2))[TestLen:]

xTVs, bin(xTVs), s0TVs, bin(s0TVs), s1TVs, bin(s1TVs)
```

```
Out[39]: (intbv(87399),
          '10101010101100111',
          intbv(52982),
          '1100111011110110',
          intbv(16277),
          '11111110010101')
```

```

In [40]: @block
          ▼ def DEMUX1_4_DMS_TBV():
              """
              myHDL -> testbench for module `DEMUX1_4_DMS`
              """

              x=Signal(bool(0))
              s0=Signal(bool(0))
              s1=Signal(bool(0))
              y0=Signal(bool(0))
              y1=Signal(bool(0))
              y2=Signal(bool(0))
              y3=Signal(bool(0))

              @always_comb
              ▼ def print_data():
                  print(x, s0, s1, y0, y1, y2, y3)

              #Test Signal Bit Vectors

              xTV=Signal(xTVs)
              s0TV=Signal(s0TVs)
              s1TV=Signal(s1TVs)

              DUT=DEMUX1_4_DMS(x, s0, s1, y0, y1, y2, y3)

              @instance
              ▼ def stimules():
                  ▼ for i in range(TestLen):
                      x.next=int(xTV[i])
                      s0.next=int(s0TV[i])
                      s1.next=int(s1TV[i])

                      yield delay(1)

                      raise StopSimulation()

              return instances()

              TB=DEMUX1_4_DMS_TBV()
              TB.convert(hdl="Verilog", initial_values=True)
              VerilogTextReader('DEMUX1_4_DMS_TBV');

```

```

<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from DEMUX1_4_DMS_TBV.v***

```

```

// File: DEMUX1_4_DMS_TBV.v
// Generated by MyHDL 0.10
// Date: Sun Sep 23 18:24:21 2018

```

```

`timescale 1ns/10ps

module DEMUX1_4_DMS_TBV (
);
// 1 Channel Input:4 Channel Output demultiplexer in Gate Level Logic

```

▼ 6.5 PYNQ-Z1 Deployment

▼ 6.5.1 Board Circuit

See Board Circuit for "1 Channel Input:4 Channel Output demultiplexer in Gate Level Logic"

▼ 6.5.2 Board Constraint

uses same 'DEMUX1_4.xdc' as "# 1 Channel Input:4 Channel Output demultiplexer in Gate Level Logic"

▼ 6.5.3 Video of Deployment

DEMUX1_4_DMS on PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=8A9iDf4nh74\)](https://www.youtube.com/watch?v=8A9iDf4nh74))

▼ 7 1:2 DEMUX via Behavioral IF

▼ 7.1 myHDL Module

```
In [41]: @block
def DEMUX1_2_B(x, s, y0, y1):
    """
    1:2 DMUX in behavioral
    Inputs:
        x(bool): input feed
        s(bool): channel select
    Outputs:
        y0(bool): ouput channel 0
        y1(bool): ouput channel 1
    """

    @always_comb
    def logic():
        if s==0:
            #take note that since we have
            #two ouputs there next state values
            #must both be set, else the last
            #value will presist till it changes
            y0.next=x
            y1.next=0
        else:
            y0.next=0
            y1.next=x

    return instances()
```

▼ 7.2 myHDL Testing

```
In [42]: TestLen=10
SystematicVals=list(itertools.product([0,1], repeat=2))

xTVs=np.array([i[1] for i in SystematicVals]).astype(int)
np.random.seed(15)
xTVs=np.append(xTVs, np.random.randint(0,2, TestLen)).astype(int)

sTVs=np.array([i[0] for i in SystematicVals]).astype(int)
#the random genrator must have a differint seed between each generation
#call in order to produce differint values for each call
np.random.seed(16)
sTVs=np.append(sTVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(xTVs)
SystematicVals, sTVs, xTVs
```

```
Out[42]: ((0, 0), (0, 1), (1, 0), (1, 1)),
array([0, 0, 1, 1, 1, 0, 1, 1, 1, 1, 0, 1, 1, 0]),
array([0, 1, 0, 1, 0, 1, 0, 1, 1, 0, 0, 1, 1, 1])
```

```

In [43]: Peeker.clear()
x=Signal(bool(0)); Peeker(x, 'x')
s=Signal(bool(0)); Peeker(s, 's')
y0=Signal(bool(0)); Peeker(y0, 'y0')
y1=Signal(bool(0)); Peeker(y1, 'y1')

DUT=DEMUX1_2_B(x, s, y0, y1)

▼ def DEMUX1_2_B_TB():
    """
    myHDL only testbench for module `DEMUX1_2_B`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            x.next=int(xTVs[i])
            s.next=int(sTVs[i])

            yield delay(1)

            raise StopSimulation()

        return instances()


sim=Simulation(DUT, DEMUX1_2_B_TB(), *Peeker.instances()).run()

```

```

In [44]: Peeker.to_wavedrom('x', 's', 'y0','y1')

```

 

```
In [45]: DEMUX1_2_BData=Peeker.to_dataframe()  
DEMUX1_2_BData=DEMUX1_2_BData[['x', 's', 'y0','y1']]  
DEMUX1_2_BData
```

Out[45]:

	x	s	y0	y1
0	0	0	0	0
1	1	0	1	0
2	0	1	0	0
3	1	1	0	1
4	0	1	0	0
5	1	0	1	0
6	0	1	0	0
7	1	1	0	1
9	0	1	0	0
10	0	0	0	0
11	1	1	0	1
13	1	0	1	0

```
In [46]: Test=DEMUX1_2_BData==DEMUX1_2_ComboData[['x', 's', 'y0','y1']]  
Test=Test.all().all()  
print(f'DEMUX1_2_BD is equivlent to DEMUX1_2_Combo: {Test}')
```

DEMUX1_2_BD is equivlent to DEMUX1_2_Combo: True

▼ 7.3 Verilog Conversion

```
In [47]: DUT.convert()  
VerilogTextReader('DEMUX1_2_B');
```

```
***Verilog modular from DEMUX1_2_B.v***
```

```
// File: DEMUX1_2_B.v  
// Generated by MyHDL 0.10  
// Date: Sun Sep 23 18:24:23 2018
```

```
`timescale 1ns/10ps
```

```
module DEMUX1_2_B (  
    x,  
    s,  
    y0,  
    y1  
);  
// 1:2 DMUX in behavioral  
// Inputs:  
//     x(bool): input feed  
//     s(bool): channel select  
// Outputs:  
//     y0(bool): ouput channel 0  
//     y1(bool): ouput channel 1
```

```
input x;  
input s;  
output y0;  
reg y0;  
output y1;  
reg y1;
```

```
always @(s, x) begin: DEMUX1_2_B_LOGIC  
    if ((s == 0)) begin  
        y0 = x;  
        y1 = 0;  
    end  
    else begin  
        y0 = 0;  
        y1 = x;  
    end  
end  
endmodule
```

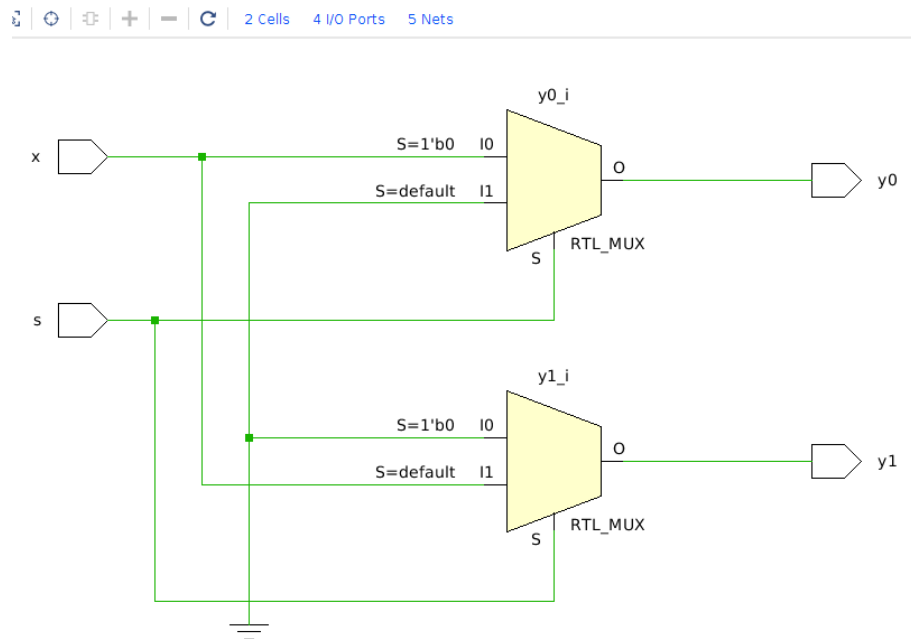


Figure 13: DEMUX1_2_B RTL schematic; Xilinx Vivado 2017.4

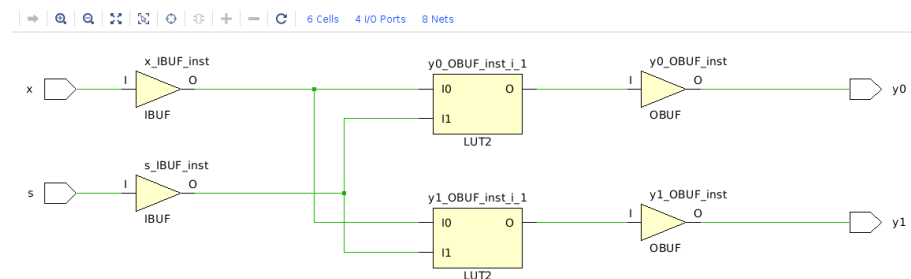


Figure 14: DEMUX1_2_B Synthesized Schematic; Xilinx Vivado 2017.4

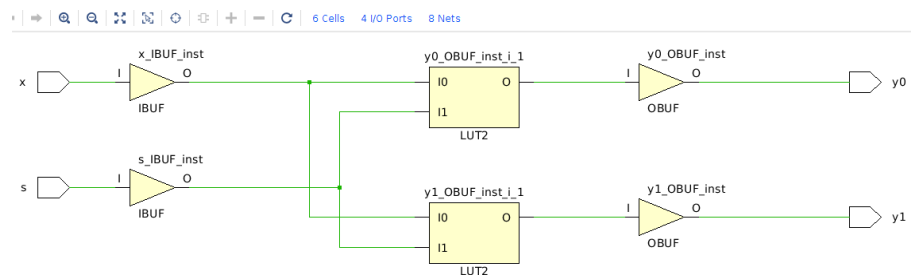


Figure 15: DEMUX1_2_B Implemented Schematic; Xilinx Vivado 2017.4

▼ 7.4 myHDL to Verilog Testbench

```
In [48]: ▼ #create BitVectors
xTVs=intbv(int(''.join(xTVs.astype(str)), 2))[TestLen:]
sTVs=intbv(int(''.join(sTVs.astype(str)), 2))[TestLen:]

xTVs, bin(xTVs), sTVs, bin(sTVs)
```

Out[48]: (intbv(5479), '1010101100111', intbv(3830), '111011110110')


```

In [49]: @block
          ▼ def DEMUX1_2_B_TBV():
              """
              myHDL -> testbench for module `DEMUX1_2_B`
              """

              x=Signal(bool(0))
              s=Signal(bool(0))
              y0=Signal(bool(0))
              y1=Signal(bool(0))

              @always_comb
              ▼ def print_data():
                  print(x, s, y0, y1)

              #Test Signal Bit Vectors

              xTV=Signal(xTVs)
              sTV=Signal(sTVs)

              DUT=DEMUX1_2_B(x, s, y0, y1)

              @instance
              ▼ def stimules():
                  ▼ for i in range(TestLen):
                      x.next=int(xTV[i])
                      s.next=int(sTV[i])

                      yield delay(1)

                      raise StopSimulation()

              return instances()

          TB=DEMUX1_2_B_TBV()
          TB.convert(hdl="Verilog", initial_values=True)
          VerilogTextReader('DEMUX1_2_B_TBV');

```

```

<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from DEMUX1_2_B_TBV.v***

```

```

// File: DEMUX1_2_B_TBV.v
// Generated by MyHDL 0.10
// Date: Sun Sep 23 18:24:23 2018

```

```

`timescale 1ns/10ps

```

```

module DEMUX1_2_B_TBV (

```

```

);
// myHDL -> testbench for module `DEMUX1_2_B`

```

```

reg x = 0;
reg s = 0;
reg y0 = 0;
reg y1 = 0;
wire [13:0] xTV;
wire [13:0] sTV;

assign xTV = 14'd5479;
assign sTV = 14'd3830;

always @(x, y0, s, y1) begin: DEMUX1_2_B_TBV_PRINT_DATA
    $write("%h", x);
    $write(" ");
    $write("%h", s);
    $write(" ");
    $write("%h", y0);
    $write(" ");
    $write("%h", y1);
    $write("\n");
end

always @(s, x) begin: DEMUX1_2_B_TBV_DEMUX1_2_B0_0_LOGIC
    if ((s == 0)) begin
        y0 = x;
        y1 = 0;
    end
    else begin
        y0 = 0;
        y1 = x;
    end
end

initial begin: DEMUX1_2_B_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        x <= xTV[i];
        s <= sTV[i];
        # 1;
    end
    $finish;
end

endmodule

```

```

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: xTV
  category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: sTV
  category=ToVerilogWarning

```

▼ 7.5 PYNQ-Z1 Deployment

▼ 7.5.1 Board Circuit

See Board Circuit for "1 Channel Input: 2 Channel Output demultiplexer in Gate Level Logic"

▼ 7.5.2 Board Constraint

uses same 'DEMUX1_2.xdc' as "1 Channel Input: 2 Channel Output demultiplexer in Gate Level Logic"

▼ 7.5.3 Video of Deployment

DEMUX1_2_B on PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=Ux0olpi2ppl\)](https://www.youtube.com/watch?v=Ux0olpi2ppl))

▼ 8 1:4 DEMUX via Behavioral if-elif-else

▼ 8.1 myHDL Module

```

In [50]: @block
▼ def DEMUX1_4_B(x, s0, s1, y0, y1, y2, y3):
    """
    1:4 DEMUX written via behaviorial

    Inputs:
        x(bool): input feed
        s0(bool): channel select 0
        s1(bool): channel select 1

    Outputs:
        y0(bool): ouput channel 0
        y1(bool): ouput channel 1
        y2(bool): ouput channel 2
        y3(bool): ouput channel 3
    """

    @always_comb
    ▼ def logic():
        ▼ if s0==0 and s1==0:
            y0.next=x; y1.next=0
            y2.next=0; y3.next=0

        ▼ elif s0==1 and s1==0:
            y0.next=0; y1.next=x
            y2.next=0; y3.next=0

        ▼ elif s0==0 and s1==1:
            y0.next=0; y1.next=0
            y2.next=x; y3.next=0

        ▼ else:
            y0.next=0; y1.next=0
            y2.next=0; y3.next=x

    return instances()

```

▼ 8.2 myHDL Testing

```

In [51]: TestLen=10
          SystmaticVals=list(itertools.product([0,1], repeat=3))

          xTVs=np.array([i[2] for i in SystmaticVals]).astype(int)
          np.random.seed(15)
          xTVs=np.append(xTVs, np.random.randint(0,2, TestLen)).astype(int)

          s0TVs=np.array([i[1] for i in SystmaticVals]).astype(int)
          #the random genrator must have a differint seed beween each generation
          #call in order to produce differint values for each call
          np.random.seed(16)
          s0TVs=np.append(s0TVs, np.random.randint(0,2, TestLen)).astype(int)

          s1TVs=np.array([i[0] for i in SystmaticVals]).astype(int)
          #the random genrator must have a differint seed beween each generation
          #call in order to produce differint values for each call
          np.random.seed(17)
          s1TVs=np.append(s1TVs, np.random.randint(0,2, TestLen)).astype(int)

          TestLen=len(xTVs)
          SystmaticVals, xTVs, s0TVs, s1TVs

```

```

Out[51]: ([ (0, 0, 0),
             (0, 0, 1),
             (0, 1, 0),
             (0, 1, 1),
             (1, 0, 0),
             (1, 0, 1),
             (1, 1, 0),
             (1, 1, 1)],
           array([0, 1, 0, 1, 0, 1, 0, 1, 0, 1, 0, 1, 1, 0, 0, 1, 1, 1]),
           array([0, 0, 1, 1, 0, 0, 1, 1, 1, 0, 1, 1, 1, 1, 0, 1, 1, 0]),
           array([0, 0, 0, 0, 1, 1, 1, 1, 1, 1, 1, 0, 0, 1, 0, 1, 0, 1]))

```

```

In [52]: Peeker.clear()
x=Signal(bool(0)); Peeker(x, 'x')
s0=Signal(bool(0)); Peeker(s0, 's0')
s1=Signal(bool(0)); Peeker(s1, 's1')
y0=Signal(bool(0)); Peeker(y0, 'y0')
y1=Signal(bool(0)); Peeker(y1, 'y1')
y2=Signal(bool(0)); Peeker(y2, 'y2')
y3=Signal(bool(0)); Peeker(y3, 'y3')

DUT=DEMUX1_4_B(x, s0, s1, y0, y1, y2, y3)

▼ def DEMUX1_4_B_TB():
    """
    myHDL only testbench for module `DEMUX1_4_Combo`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            x.next=int(xTVs[i])
            s0.next=int(s0TVs[i])
            s1.next=int(s1TVs[i])

            yield delay(1)

            raise StopSimulation()

        return instances()


sim=Simulation(DUT, DEMUX1_4_B_TB(), *Peeker.instances()).run()

```

```

In [53]: Peeker.to_wavedrom('x', 's1', 's0', 'y0', 'y1', 'y2', 'y3')

```

 

```
In [54]: DEMUX1_4_BData=Peeker.to_dataframe()
DEMUX1_4_BData=DEMUX1_4_BData[['x', 's1', 's0', 'y0', 'y1', 'y2', 'y3']]
DEMUX1_4_BData
```

Out[54]:

	x	s1	s0	y0	y1	y2	y3
0	0	0	0	0	0	0	0
1	1	0	0	1	0	0	0
2	0	0	1	0	0	0	0
3	1	0	1	0	1	0	0
4	0	1	0	0	0	0	0
5	1	1	0	0	0	1	0
6	0	1	1	0	0	0	0
7	1	1	1	0	0	0	1
8	0	1	1	0	0	0	0
9	1	1	0	0	0	1	0
10	0	1	1	0	0	0	0
11	1	0	1	0	1	0	0
13	0	1	1	0	0	0	0
14	0	0	0	0	0	0	0
15	1	1	1	0	0	0	1
16	1	0	1	0	1	0	0
17	1	1	0	0	0	1	0

```
In [55]: Test=DEMUX1_4_BData==DEMUX1_4_ComboData[['x', 's1', 's0', 'y0', 'y1', 'y2', 'y3']]
Test=Test.all().all()
print(f'DEMUX1_4_B equivlinet to DEMUX1_4_Combo: {Test}')
```

DEMUX1_4_B equivlinet to DEMUX1_4_Combo: True

▼ 8.3 Verilog Conversion

```
In [56]: DUT.convert()  
VerilogTextReader('DEMUX1_4_B');
```

```
***Verilog modular from DEMUX1_4_B.v***
```

```
// File: DEMUX1_4_B.v  
// Generated by MyHDL 0.10  
// Date: Sun Sep 23 18:24:25 2018
```

```
`timescale 1ns/10ps
```

```
module DEMUX1_4_B (  
    x,  
    s0,  
    s1,  
    y0,  
    y1,  
    y2,  
    y3  
);  
// 1:4 DEMUX written via behavioral  
//  
// Inputs:  
//     x(bool): input feed  
//     s0(bool): channel select 0  
//     s1(bool): channel select 1  
//  
// Outputs:  
//     y0(bool): ouput channel 0  
//     y1(bool): ouput channel 1  
//     y2(bool): ouput channel 2  
//     y3(bool): ouput channel 3  
  
input x;  
input s0;  
input s1;  
output y0;  
reg y0;  
output y1;  
reg y1;  
output y2;  
reg y2;  
output y3;  
reg y3;  
  
always @(x, s1, s0) begin: DEMUX1_4_B_LOGIC  
    if (((s0 == 0) && (s1 == 0))) begin  
        y0 = x;  
        y1 = 0;  
        y2 = 0;  
        y3 = 0;  
    end  
    else if (((s0 == 1) && (s1 == 0))) begin
```



```

        y0 = 0;
        y1 = x;
        y2 = 0;
        y3 = 0;
    end
    else if ((s0 == 0) && (s1 == 1))) begin
        y0 = 0;
        y1 = 0;
        y2 = x;
        y3 = 0;
    end
    else begin
        y0 = 0;
        y1 = 0;
        y2 = 0;
        y3 = x;
    end
end
endmodule

```

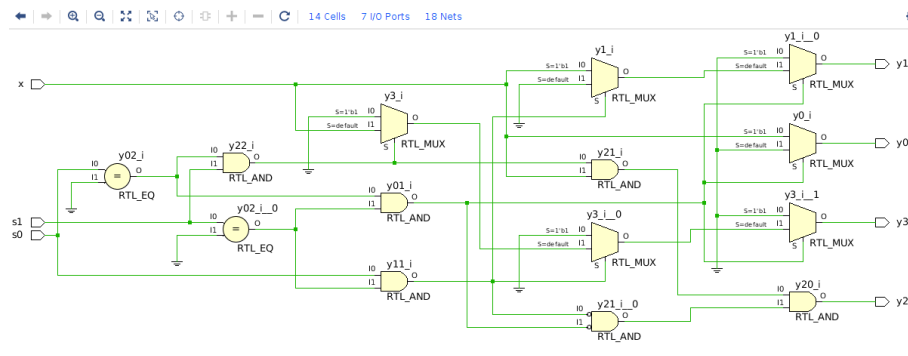


Figure 16: DEMUX1_4_B RTL schematic; Xilinx Vivado 2017.4

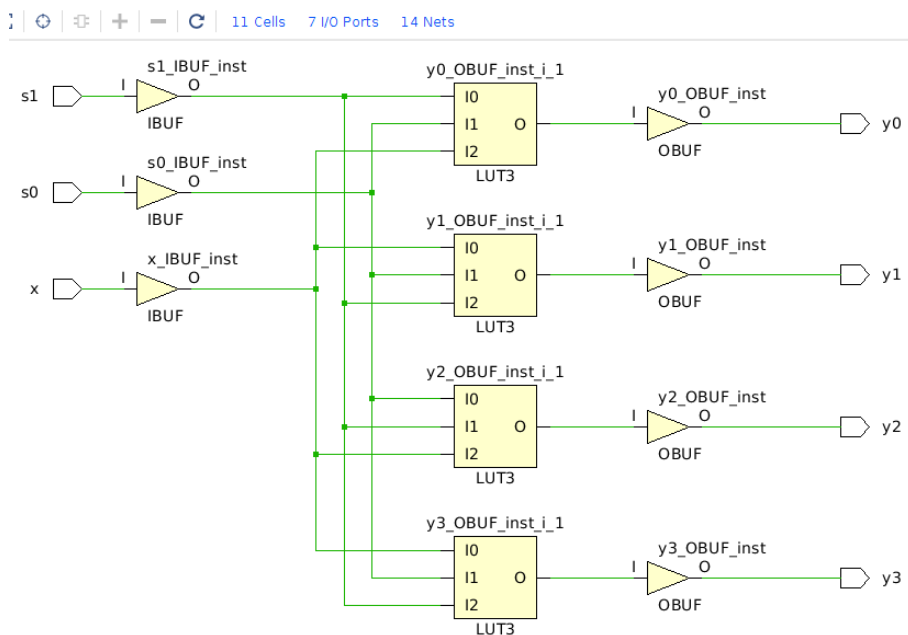


Figure 17: DEMUX1_4_B Synthesized Schematic; Xilinx Vivado 2017.4

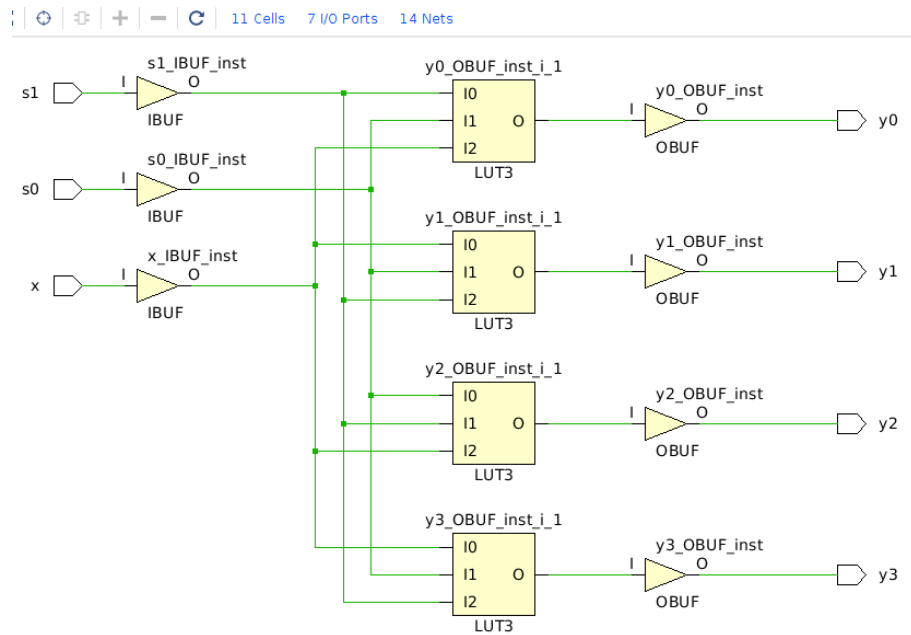


Figure 18: DEMUX1_4_B Implemented Schematic; Xilinx Vivado 2017.4

▼ 8.4 myHDL to Verilog Testbench

```
In [57]: ▼ #create BitVectors
xTVs=intbv(int(''.join(xTVs.astype(str)), 2))[TestLen:]
s0TVs=intbv(int(''.join(s0TVs.astype(str)), 2))[TestLen:]
s1TVs=intbv(int(''.join(s1TVs.astype(str)), 2))[TestLen:]
```

```
xTVs, bin(xTVs), s0TVs, bin(s0TVs), s1TVs, bin(s1TVs)
```

```
Out[57]: (intbv(87399),
'10101010101100111',
intbv(52982),
'1100111011110110',
intbv(16277),
'11111110010101')
```

```
In [58]: @block
def DEMUX1_4_B_TBV():
    """
    myHDL -> testbench for module `DEMUX1_4_B`
    """

    x=Signal(bool(0))
    s0=Signal(bool(0))
    s1=Signal(bool(0))
    y0=Signal(bool(0))
    y1=Signal(bool(0))
    y2=Signal(bool(0))
    y3=Signal(bool(0))

    @always_comb
    def print_data():
        print(x, s0, s1, y0, y1, y2, y3)

    #Test Signal Bit Vectors

    xTV=Signal(xTVs)
    s0TV=Signal(s0TVs)
    s1TV=Signal(s1TVs)

    DUT=DEMUX1_4_B(x, s0, s1, y0, y1, y2, y3)

    @instance
    def stimules():
        for i in range(TestLen):
            x.next=int(xTV[i])
            s0.next=int(s0TV[i])
            s1.next=int(s1TV[i])

            yield delay(1)

            raise StopSimulation()

        return instances()

TB=DEMUX1_4_B_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('DEMUX1_4_B_TBV');
```

```
initial begin: DEMUX1_4_B_TBV_STIMULES
    integer i;
    for (i=0; i<18; i=i+1) begin
        x <= xTV[i];
        s0 <= s0TV[i];
        s1 <= s1TV[i];
        # 1;
    end
    $finish;
end

endmodule
```

```
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_toVerilog.py:349: ToVerilogWarning: Signal is not driven: xTV
  category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_toVerilog.py:349: ToVerilogWarning: Signal is not driven: sATV
```

▼ 8.5 PYNQ-Z1 Deployment

▼ 8.5.1 Board Circuit

See Board Circuit for "1 Channel Input:4 Channel Output demultiplexer in Gate Level Logic"

▼ 8.5.2 Board Constraint

uses same 'DEMUX1_4.xdc' as "# 1 Channel Input:4 Channel Output demultiplexer in Gate Level Logic"

▼ 8.5.3 Video of Deployment

DEMUX1_4_B on PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=MezWijKoDuk\)](https://www.youtube.com/watch?v=MezWijKoDuk))

▼ 9 Demultiplexer 1:4 Behavioral via Bitvectors

▼ 9.1 myHDL Module

```

In [59]: @block
def DEMUX1_4_BV(x, S, Y):
    """
    1:4 DEMUX written via behavioral with
    bit vectors

    Inputs:
        x(bool): input feed
        S(2bit vector): channel select bitvector;
            min=0, max=3

    Outputs:
        Y(4bit vector): ouput channel bitvector;
            values min=0, max=15; allowed is: 0,1,2,4,8
            in this application

    """

    @always_comb
    def logic():
        #here concat is used to build up the word
        #from the x input
        if S==0:
            Y.next=concat(intbv(0)[3:], x); '0001'
        elif S==1:
            Y.next=concat(intbv(0)[2:], x, intbv(0)[1:]); '0010'
        elif S==2:
            Y.next=concat(intbv(0)[1:], x, intbv(0)[2:]); '0100'
        else:
            Y.next=concat(x, intbv(0)[3:]); '1000'

    return instances()

```

▼ 9.2 myHDL Testing

```

In [60]: xTVs=np.array([0,1])
xTVs=np.append(xTVs, np.random.randint(0,2,6)).astype(int)
TestLen=len(xTVs)

np.random.seed(12)
STVs=np.arange(0,4)
STVs=np.append(STVs, np.random.randint(0,4, 5))
TestLen, xTVs, STVs

```

```

Out[60]: (8, array([0, 1, 0, 1, 0, 0, 1, 1]), array([0, 1, 2, 3, 3, 3, 2, 1,
1]))

```

```
In [61]: Peeker.clear()
x=Signal(bool(0)); Peeker(x, 'x')
S=Signal(intbv(0)[2:]); Peeker(S, 'S')
Y=Signal(intbv(0)[4:]); Peeker(Y, 'Y')

DUT=DEMUX1_4_BV(x, S, Y)


▼ def DEMUX1_4_BV_TB():
    @instance
    ▼ def stimules():
        ▼ for i in STVs:
            ▼ for j in xTVs:
                S.next=int(i)
                x.next=int(j)
                yield delay(1)

            raise StopSimulation()

    return instances()

sim=Simulation(DUT, DEMUX1_4_BV_TB(), *Peeker.instances()).run()
```
 
```
In [63]: Peeker.to_wavedrom('x', 'S', 'Y', start_time=0, stop_time=2*TestLen+2)
```



```
In [66]: DEMUX1_4_BVData=Peeker.to_dataframe()
DEMUX1_4_BVData=DEMUX1_4_BVData[['x', 'S', 'Y']]
DEMUX1_4_BVData
```

Out[66]:

	x	S	Y
0	0	0	0
1	1	0	1
2	0	0	0
3	1	0	1
4	0	0	0
6	1	0	1
8	0	1	0
9	1	1	2
10	0	1	0
11	1	1	2
12	0	1	0

```
In [67]: DEMUX1_4_BVData['y0']=None; DEMUX1_4_BVData['y1']=None; DEMUX1_4_BVData
DEMUX1_4_BVData[['y3', 'y2', 'y1', 'y0']]=DEMUX1_4_BVData[['Y']].apply(

DEMUX1_4_BVData['s0']=None; DEMUX1_4_BVData['s1']=None
DEMUX1_4_BVData[['s1', 's0']]=DEMUX1_4_BVData[['S']].apply(lambda bv: [

DEMUX1_4_BVData=DEMUX1_4_BVData[['x', 'S', 's0', 's1', 'Y', 'y3', 'y2',
DEMUX1_4_BVData
```

```
46 1 3 1 1 8 1 0 0 0
48 0 2 0 1 0 0 0 0 0
49 1 2 0 1 4 0 1 0 0
50 0 2 0 1 0 0 0 0 0
51 1 2 0 1 4 0 1 0 0
52 0 2 0 1 0 0 0 0 0
54 1 2 0 1 4 0 1 0 0
56 0 1 1 0 0 0 0 0 0
57 1 1 1 0 2 0 0 1 0
58 0 1 1 0 0 0 0 0 0
59 1 1 1 0 2 0 0 1 0
60 0 1 1 0 0 0 0 0 0
62 1 1 1 0 2 0 0 1 0
```

```
In [70]: DEMUX1_4_BVData['y0Ref']=DEMUX1_4_BVData.apply(lambda row:y14_0EqN(row|
DEMUX1_4_BVData['y1Ref']=DEMUX1_4_BVData.apply(lambda row:y14_1EqN(row|
DEMUX1_4_BVData['y2Ref']=DEMUX1_4_BVData.apply(lambda row:y14_2EqN(row|
DEMUX1_4_BVData['y3Ref']=DEMUX1_4_BVData.apply(lambda row:y14_3EqN(row|
```

DEMUX1_4_BVData

16	0	2	0	1	0	0	0	0	0	0	0	0	0
17	1	2	0	1	4	0	1	0	0	0	0	1	0
18	0	2	0	1	0	0	0	0	0	0	0	0	0
19	1	2	0	1	4	0	1	0	0	0	0	1	0
20	0	2	0	1	0	0	0	0	0	0	0	0	0
22	1	2	0	1	4	0	1	0	0	0	0	1	0
24	0	3	1	1	0	0	0	0	0	0	0	0	0
25	1	3	1	1	8	1	0	0	0	0	0	0	1
26	0	3	1	1	0	0	0	0	0	0	0	0	0
27	1	3	1	1	8	1	0	0	0	0	0	0	1
28	0	3	1	1	0	0	0	0	0	0	0	0	0
30	1	3	1	1	8	1	0	0	0	0	0	0	1
32	0	3	1	1	0	0	0	0	0	0	0	0	0

```
In [84]: X1_4_BVData[['y0', 'y1', 'y2', 'y3']].sort_index(inplace=True)==DEMUX1_4_
Module `DEMUX1_4_BVData` works as expected: {Test}')
```

Module `DEMUX1_4_BVData` works as expected: True

▼ 9.3 Verilog Conversion

In [85]:

```
DUT.convert()  
VerilogTextReader('DEMUX1_4_BV');
```

```
***Verilog modular from DEMUX1_4_BV.v***  
  
// File: DEMUX1_4_BV.v  
// Generated by MyHDL 0.10  
// Date: Sun Sep 23 18:48:43 2018  
  
`timescale 1ns/10ps  
  
module DEMUX1_4_BV (  
    x,  
    S,  
    Y  
);  
// 1:4 DEMUX written via behavioral with  
// bit vectors  
//  
// Inputs:  
//     x(bool): input feed  
//     S(2bit vector): channel select bitvector;  
//         min=0, max=3  
//  
// Outputs:  
//     Y(4bit vector): ouput channel bitvector;  
//         values min=0, max=15; allowed is: 0,1,2,4,8  
//         in this application  
//  
  
input x;  
input [1:0] S;  
output [3:0] Y;  
reg [3:0] Y;  
  
always @(x, S) begin: DEMUX1_4_BV_LOGIC  
    case (S)  
        'h0: begin  
            Y = {3'h0, x};  
            // 0001  
        end  
        'h1: begin  
            Y = {2'h0, x, 1'h0};  
            // 0010  
        end  
        'h2: begin  
            Y = {1'h0, x, 2'h0};  
            // 0100  
        end  
        default: begin  
            Y = {x, 3'h0};  
            // 1000  
        end  
    end  
end
```

```

        endcase
    end

endmodule

```

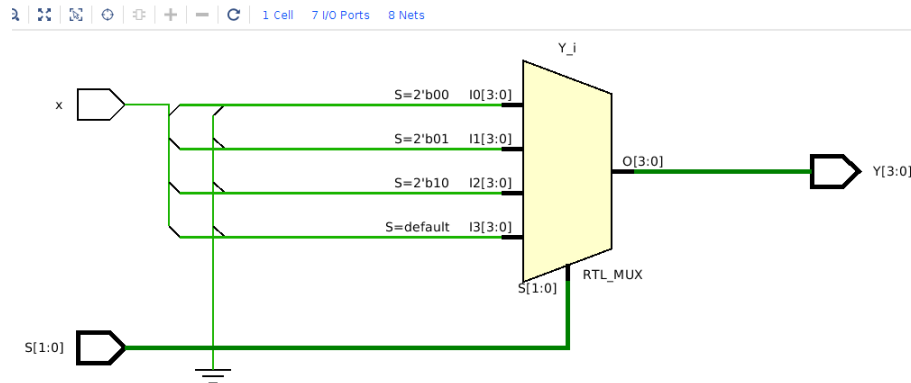


Figure 19: DEMUX1_4_BV RTL schematic; Xilinx Vivado 2017.4


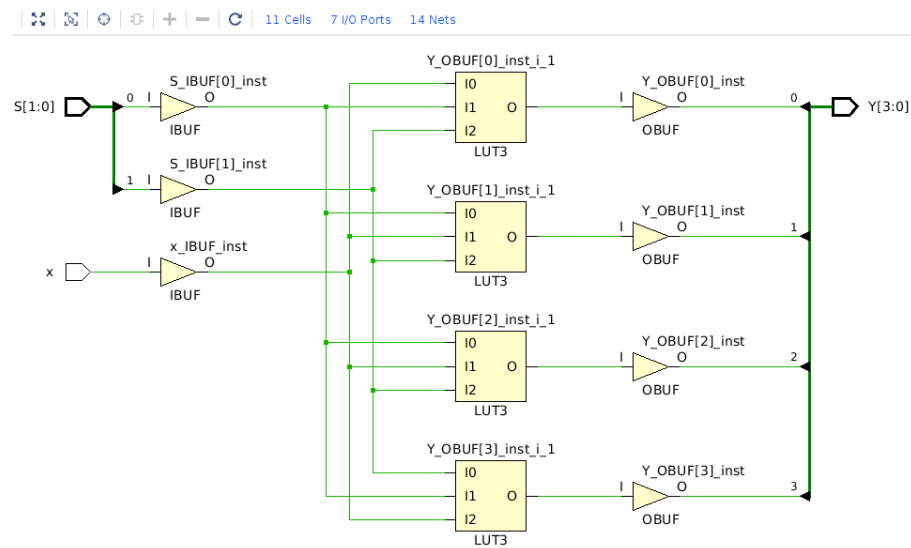


Figure 20: DEMUX1_4_BV Synthesized Schematic; Xilinx Vivado 2017.4

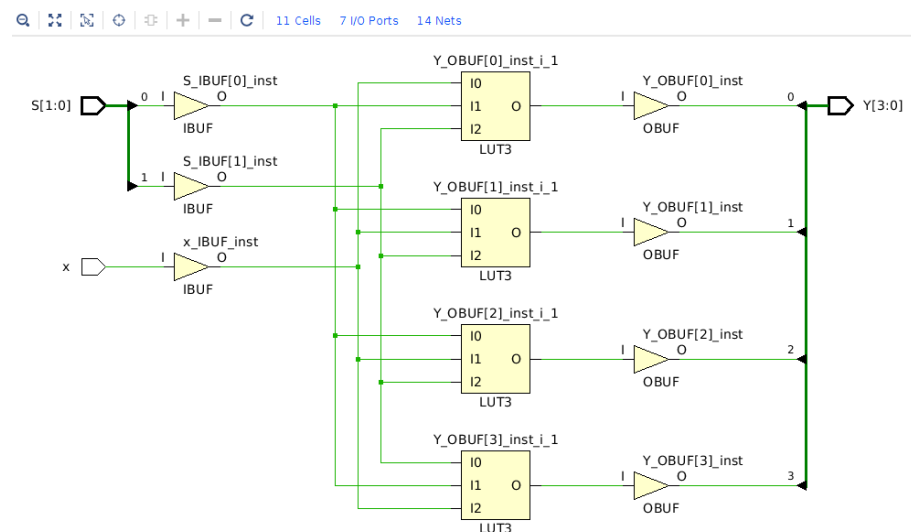

▼ 9.4 myHDL to Verilog Testbench

(To Do!)

▼ 9.5 PYNQ-Z1 Board Deployment

▼ 9.5.1 Board Circuit

▼ 9.5.2 Board Constraints

```
In [86]: ConstraintXDCTextReader('DEMUX1_4_BV');

***Constraint file from DEMUX1_4_BV.xdc***

## Switches
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {S
[0]}}; ##SW0
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {S
[1]}}; ##SW1

## Buttons

set_property -dict {PACKAGE_PIN L19 IOSTANDARD LVCMOS33} [get_ports
{x]}; ##BT3

## RGBLEDs
set_property -dict { PACKAGE_PIN L15      IOSTANDARD LVCMOS33 } [get_ports
{Y[0]}}; ##LD4_Blue
set_property -dict { PACKAGE_PIN G17      IOSTANDARD LVCMOS33 } [get_ports
{Y[1]}}; ##LD4_Green
set_property -dict { PACKAGE_PIN L14      IOSTANDARD LVCMOS33 } [get_ports
{Y[2]}}; ##LD5_Green
set_property -dict { PACKAGE_PIN M15      IOSTANDARD LVCMOS33 } [get_ports
{Y[3]}}; ##LD5_Red
```

▼ 9.5.3 Video of Deployment

DEMUX1_4_BV on PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=mVyTlkbJpKg\)](https://www.youtube.com/watch?v=mVyTlkbJpKg))