

Logic Gate Primitives in myHDL

Steven K Armour

Table of Contents

- [1 Libraries and Helper functions](#)
- [2 Table of Digital Gate Symbols commonly used](#)
- [3 How to load output Verilog from myHDL to Xilinx's Vivado](#)
- [4 Wire High](#)
 - [4.1 Sympy Exspresion](#)
 - [4.2 myHDL Module](#)
 - [4.3 Verilog Conversion](#)
 - [4.4 PYNQ-Z1 Deployment](#)
 - [4.4.1 Board Circuit](#)
 - [4.4.2 Board Constraint](#)
- [5 Wire Low](#)
 - [5.1 Sympy Expression](#)
 - [5.2 myHDL Module](#)
 - [5.3 Verilog Conversion](#)
 - [5.4 PYNQ-Z1 Deployment](#)
 - [5.4.1 Board Circuit](#)
 - [5.4.2 Board Constraint](#)
- [6 Buffer](#)
 - [6.1 Sympy Expression](#)
 - [6.2 myHDL Module](#)
 - [6.3 myHDL Testing](#)
 - [6.4 Verilog Conversion](#)
 - [6.5 myHDL to Verilog Testbench](#)
 - [6.6 PYNQ-Z1 Deployment](#)
 - [6.6.1 Board Circuit](#)

▼ 1 Libraries and Helper functions

```
In [1]: #This notebook also uses the `(some) LaTeX environments for Jupyter`
#https://github.com/ProfFan/latex_envs wich is part of the
#jupyter_contrib_nbextensions package

from myhdl import *
from myhdlpeek import Peeker
import numpy as np
import pandas as pd
import matplotlib.pyplot as plt
%matplotlib inline

from sympy import *
init_printing()

import itertools

#EE drawing tools in python from https://cdelker.bitbucket.io/SchemDraw
import SchemDraw as schem
import SchemDraw.elements as e
import SchemDraw.logic as l

#https://github.com/jrjohansson/version_information
%load_ext version_information
%version_information myhdl, myhdlpeek, numpy, pandas, matplotlib, sympy
```

```
Out[1]:
```

Software	Version
Python	3.6.2 64bit [GCC 4.4.7 20120313 (Red Hat 4.4.7-1)]
IPython	6.2.1
OS	Linux 4.15.0 30 generic x86_64 with debian stretch sid
myhdl	0.10
myhdlpeek	0.0.6
numpy	1.13.3
pandas	0.23.3
matplotlib	2.1.0
sympy	1.1.2.dev
itertools	The 'itertools' distribution was not found and is required by the application
SchemDraw	0.3.0

Mon Sep 03 14:42:23 2018 MDT

```
In [2]: #helper functions to read in the .v and .vhd generated files into python
def VerilogTextReader(loc, printresult=True):
    with open(f'{loc}.v', 'r') as vText:
        VerilogText=vText.read()
    if printresult:
        print(f'***Verilog modual from {loc}.v***\n\n', VerilogText)
    return VerilogText

def VHDLTextReader(loc, printresult=True):
    with open(f'{loc}.vhd', 'r') as vText:
        VerilogText=vText.read()
    if printresult:
        print(f'***VHDL modual from {loc}.vhd***\n\n', VerilogText)
    return VerilogText

def ConstraintXDCTextReader(loc, printresult=True):
    with open(f'{loc}.xdc', 'r') as xdcText:
        ConstraintText=xdcText.read()
    if printresult:
        print(f'***Constraint file from {loc}.xdc***\n\n', ConstraintText)
    return ConstraintText
```

```
In [3]: def TruthTabelGenrator(BoolSymFunc):
    """
    Function to generate a truth table from a sympy boolian expression
    BoolSymFunc: sympy boolian expression
    return TT: a Truth table stored in a pandas dataframe
    """
    colsL=sorted([i for i in list(BoolSymFunc.rhs.atoms())], key=lambda x: x.sort_key())
    colsR=sorted([i for i in list(BoolSymFunc.lhs.atoms())], key=lambda x: x.sort_key())
    bitwidth=len(colsL)
    cols=colsL+colsR; cols

    TT=pd.DataFrame(columns=cols, index=range(2**bitwidth))

    for i in range(2**bitwidth):
        inputs=[int(j) for j in list(np.binary_repr(i, bitwidth))]
        outputs=BoolSymFunc.rhs.subs({j:v for j, v in zip(colsL, inputs)})
        inputs.append(int(bool(outputs)))
        TT.iloc[i]=inputs

    return TT
```

▼ 2 Table of Digital Gate Symbols commonly used

Logic function	American (MIL/ANSI) Symbol	British (BS3939) Symbol	Common German Symbol	International Electrotechnical Commission (IEC) Symbol
	IN OUT	IN OUT	IN OUT	IN OUT
Buffer				
Inverter (NOT gate)				
2-input AND gate				
2-input NAND gate				
2-input OR gate				
2-input NOR gate				
2-input EX-OR gate				
2-input EX-NOR gate				

Figure 1: Table of selected Logic Gate Symbols found worldwide;

▼ 3 How to load output Verilog from myHDL to Xilinx's Vivado

[YouTube \(https://youtu.be/K6rLsdJO2CE\)](https://youtu.be/K6rLsdJO2CE)

▼ 4 Wire High

Definition 1 \label{def:Wire High} A Wire to High is a Wire connected to the Highest reference voltage in a Digital Circuit with the Boolean equivalency of

$$Y = 1$$

that of *always True*

```
In [4]: d = schem.Drawing(unit=.5)
d.add(e.VDD, label='High')
d.add(e.LINE, l=d.unit*2, d='down')
d.add(e.DOT_OPEN, botlabel='$1$')
d.draw()
```



▼ 4.1 Sympy Exspresion

```
In [5]: Y=symbols('Y')
YEq=Eq(Y, 1); YEq
```

```
Out[5]: Y = 1
          v _ 1
```

▼ 4.2 myHDL Module

```
In [6]: ▼ #decorator to specify a myHDL module that can be converted
          #to myHDL
          @block
          ▼ def WireHigh(Y):
              """
              Wire to Constatnt High
              Input:
              None
              Output:
              Y(bool): output
              """
              #create signal to High Source
              HSource=Signal(bool(1))

              #decorator for a compintorical senstvity
              @always_comb
              ▼ def logic():
                  #internal function to specfiy Out is set to High Source
                  Y.next=HSource

              #return all internal functions
              return instances()
```

▼ 4.3 Verilog Conversion

```
In [7]: ▾ #create output signal to bind to `WireHigh` Mod
Y=Signal(bool(0))
#Create instatnce of `WireHigh` and bind `Out` Signal to it
DUT=WireHigh(Y)
#Run convert on `DUT` instance of `WireHigh` to create Verilog/VHDL
DUT.convert()
#Read ouput `WireHigh.v` into notebook
VerilogTextReader('WireHigh');
```

Verilog modual from WireHigh.v

```
// File: WireHigh.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:42:38 2018
```

```
`timescale 1ns/10ps
```

```
module WireHigh (
    Y
);
// Wire to Constatnt High
// Input:
//      None
// Output:
//      Y(bool): output
```

```
output Y;
wire Y;
```


```
wire HSource;
```

```
assign HSource = 1'd1;
```

```
assign Y = HSource;
```

```
endmodule
```
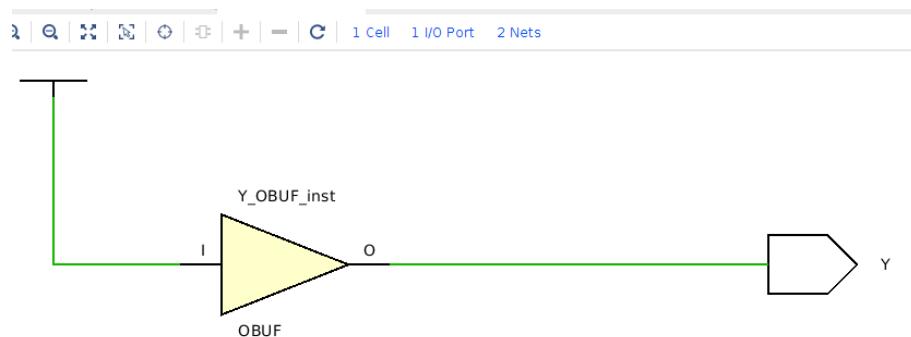
```
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: HSource
category=ToVerilogWarning
```



Processing math: 100%

Figure 2: WireHigh RTL schematic (Ignore the Buffer in the middle); Xilinx Vivado 2017.4

 


Figure 3: WireHigh Synthesized Schematic (Ignore the Buffer in the middle); Xilinx Vivado 2017.4

 



Figure 4: WireHigh Implemented Schematic (Ignore the Buffer in the middle); Xilinx Vivado 2017.4

▼ 4.4 PYNQ-Z1 Deployment

▼ 4.4.1 Board Circuit

```
In [8]: d = schem.Drawing(unit=.5)
d.add(e.VDD, label='High')
d.add(e.LINE, l=d.unit*2, d='down')
d.add(e.DOT, rgtlabel='$1$')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.LED, rgtlabel='LD0', d='down')
 
#LED to ground
d.add(e.LINE, d='down', l=d.unit*1.5)
d.add(e.GND)
d.draw()
```



▼ 4.4.2 Board Constraint

```
In [9]: ConstraintXDCTextReader('PYNQ_Z1Constraints_WireHigh');

***Constraint file from PYNQ_Z1Constraints_WireHigh.xdc***

## PYNQ-Z1 Board Constraints for WireHigh.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```

LED 0 (the furthest Right one above the buttons) will light up green

▼ 5 Wire Low

Definition 2 A Wire to Low is a Wire connected to the Lowest reference voltage in a Digital Circuit with the Boolean equivalency of

$$Y = 0$$

that of **always False**

In most modern digital circuits this Lowest reference voltage will be digital ground.


```
In [10]: d = schem.Drawing(unit=.5)
d.add(e.DOT_OPEN, label='$0$')
d.add(e.LINE, l=d.unit*2, d='down')
d.add(e.GND)
d.draw()
```



▼ 5.1 Sympy Expression

```
In [11]: Y=Symbol('Y')
YEq=Eq(Y, 0); YEq
```

```
Out[11]: Y = 0
          v - n
```

▼ 5.2 myHDL Module

```
In [12]: ▼ #decorator to specify a myHDL module that can be converted
           #to myHDL
           @block
           ▼ def WireLow(Y):
               """
               Wire to Constant Low
               ▼ Input:
                   None
               ▼ Output:
                   Y(bool): output
               """
               #create signal to Low Source
               LSource=Signal(bool(0))

               #decorator for a combinatorical sensitivity
               @always_comb
               ▼ def logic():
                   #internal function to specify Out is set to Low Source
                   Y.next=LSource

               #return all internal functions
               return instances()
```

▼ 5.3 Verilog Conversion

```
In [13]: ▾ #create output signal to bind to `WireHigh` Mod
Y=Signal(bool(0))
#Create instatnce of `WireHigh` and bind `Out` Signal to it
DUT=WireLow(Y)
#Run convert on `DUT` instance of `WireHigh` to create Verilog/VHDL
DUT.convert()
#Read ouput `WireHigh.v` into notebook
VerilogTextReader('WireLow');
```

Verilog modular from WireLow.v

```
// File: WireLow.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:43:08 2018
```

```
`timescale 1ns/10ps
```

```
module WireLow (
    Y
);
// Wire to Constatnt Low
// Input:
//     None
// Output:
//     Y(bool): output
```

```
output Y;
wire Y;
```

```
wire LSource;
```

```
assign LSource = 1'd0;
```

```
assign Y = LSource;
```

```
endmodule
```

```
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: LSource
category=ToVerilogWarning
```

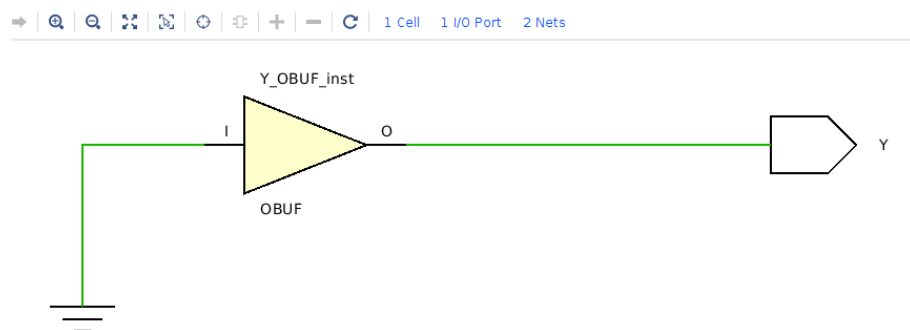


Figure 5: WireLow RTL schematic (Ignore the Buffer in the middle); Xilinx Vivado 2017.4

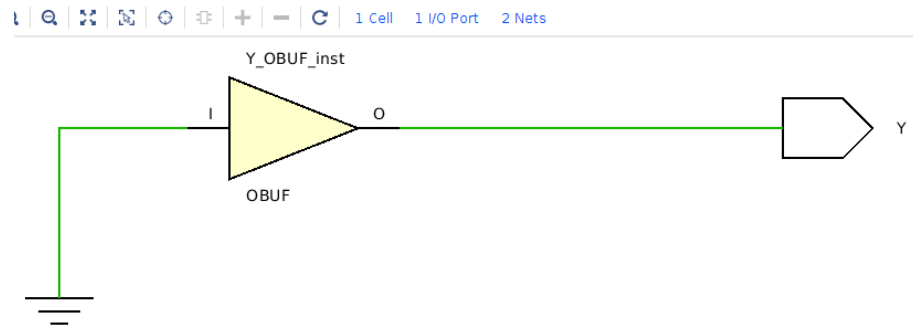


Figure 6: WireLow Synthesized Schematic (Ignore the Buffer in the middle); Xilinx Vivado 2017.4

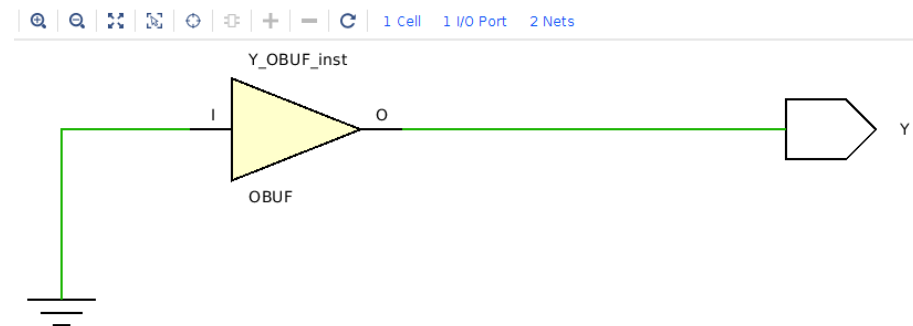



Figure 7: WireLow Implemented Schematic (Ignore the Buffer in the middle); Xilinx Vivado 2017.4

▼ 5.4 PYNQ-Z1 Deployment

▼ 5.4.1 Board Circuit

```
In [14]: d = schem.Drawing(unit=.5)
LD0=d.add(e.LED, d='right', label='LD0')
d.add(e.LINE, l=d.unit*2, d='left', xy=LD0.start)
d.add(e.LINE, l=d.unit*2, d='down')
d.add(e.GND)

 d.add(e.LINE, l=d.unit*2, d='right', xy=LD0.end)
d.add(e.LINE, l=d.unit*2, d='down')
d.add(e.GND)
d.draw()
```



▼ 5.4.2 Board Constraint

```
In [15]: ConstraintXDCTextReader('PYNQ_Z1Constraints_WireLow');

***Constraint file from PYNQ_Z1Constraints_WireLow.xdc***

## PYNQ-Z1 Board Constraints for WireHigh.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```

Nothing will happen since the Low Signal on the PYNQ-Z1 is ground so LED 0 will remain off


▼ 6 Buffer

Definition 3 A Buffer Gate is a gate whose output is one to one with its input, in both behavior and ideally in time. The Buffer Gates boolean equivalence is

$$Y = X$$

From a Boolean algebra/software perspective this may be a do-nothing gate but from a hardware perspective, it is incredibly valuable as it isolates the incoming signal circuit from any inline feedback on the outgoing signal's circuit. And is also typically used in circuit design as a way of ensuring the output of a system will be at the right voltage levels of the technology so that the next set of gates will register the input to them correctly
 
```
In [16]: d = schem.Drawing(unit=.5)
d.add(e.DOT_OPEN, l=d.unit*3, lftlabel='$X$')
d.add(l.BUF, label='$Buffer$')
d.add(e.DOT_OPEN, l=d.unit*2, rgtlabel='$Y$')
d.draw()
```



▼ 6.1 Sympy Expression

```
In [17]: X, Y=symbols('X, Y')
YEq=Eq(Y, X); YEq
```

```
Out[17]: Y = X
```

```
In [18]: TruthTabelGenrator(YEq)
```

```
Out[18]:
```

	X	Y
0	0	0
1	1	1

```
In [19]: ▼ #convert the Sympy expsresion to a
#numpy expsresion via lambdify
YEqN=lambdify(X, YEq.rhs, dummify=False)
YEqN(np.array([0, 1]))
```

```
Out[19]: array([0, 1])
```

▼ 6.2 myHDL Module

```
In [20]: @block
▼ def BufferGate(X, Y):
    """
    Buffer Gate demo module
    Input:
    ▼ X(bool): Input conection to wire between `X` and `Y`
    ▼ Output:
    Y(bool): Output connection to wire between 'X' and 'Y'
    """
    @always_comb
    ▼ def logic():
        Y.next=X
    return instances()
```

6.3 myHDL Testing

Every module (WireHigh and WireLow are just too primitive to test) should be tested with a Testbench in python. This test does not confirm that the module meets the requirements of synthesization in Verilog/VHDL but confirms that the behavior of the myHDL module under test (DUT) behavior wise conforms to the desired behavior.

Because of the data analysis ability of python to full analysis the test output in the same framework that the test, let alone module, was written in development time is decreased. This is one of the defining abilities of myHDL over other HDLs such as Verilog/VHDL

Synthesization in the world of HDL refers to the ability to turn HDL code into Hardware via an FPGA or a dedicated circuit (typically called an ASIC). It is for that reason that HDL codeing is not pure software nor pure hardware but rather a hybrid of the two. And why HDL coding has high constraints then all other coding seeing as the HDL must meet Behavior and Timing of software but must also meet the hardware synthesis requirements of Power, Physical Size, Implantability, and more

```
In [21]: #generate random test values for BufferGate_TB  
#stimules input In  
TestLen=10  
#for testing purpose the random genrator need to be seeded  
#to create reproducible values  
np.random.seed(12)  
XTVs=np.random.randint(0,2, TestLen).astype(int)  
XTVs
```

```
Out[21]: array([1, 1, 0, 1, 1, 0, 1, 1, 0, 0])
```

```

In [22]: ▾ #clear any previous stored values in Peeker
Peeker.clear()
#Create the Signals to the BufferGate and
#add them to Peeker for display and anylis
X=Signal(bool(0)); Peeker(X, 'X')
Y=Signal(bool(0)); Peeker(Y, 'Y')

#create instance of `BufferGate` and bind signals
#to it as the "Device Under Testing"
DUT=BufferGate(X, Y)

#Create a Testbench for `BufferGate`
▾ def BufferGate_TB():
    """
    myHDL only testbench for module `BufferGate`
    """
    #internal function that will apply
    #stimules to DUT
    @instance
    ▾ def stimules():
        ▾ for i in range(TestLen):
            #assign next stimules value to X input of DUT
            #for every 1 interval delay
            X.next=int(XTVs[i])
            yield delay(1)

            #flag to end the simulation of the DUT after all
            #stimules have been run
            raise StopSimulation()

    #return all internal stimules
    return instances()

#bind the DUT, Testbench and Peeker to simulator and run it
sim=Simulation(DUT, BufferGate_TB(), *Peeker.instances()).run()

```

```

In [23]: ▾ #View Waveform diagram from Simulation with
#waveforms in the order of `X` then `Y`
Peeker.to_wavedrom('X', 'Y')

```

```
In [24]: ▼ #Capture the Waveform as a Pandas Dataframe for
#detailed anylsis
WireData=Peeker.to_dataframe()
#order the cols in the dataframe `X` then `Y`
WireData=WireData[['X', 'Y']]
WireData
```

```
Out[24]:
```

	X	Y
0	1	1
2	0	0
3	1	1
5	0	0
6	1	1
8	0	0

```
In [25]: ▼ #apply the lampdfid sympy expspresion for a buffer to the X input to
#get a refrance to compare the BufferGate modules
WireData['YRef']=WireData['X'].apply(YEqN)
WireData
```

```
Out[25]:
```

	X	Y	YRef
0	1	1	1
2	0	0	0
3	1	1	1
5	0	0	0
6	1	1	1
8	0	0	0

```
In [26]: ▼ #Test wither the modules ouput matchs the sympy refrance
Test=(WireData['Y']==WireData['YRef']).all()
print(f'Module `BufferGate` works as exspected: {Test}')
```

Module `BufferGate` works as exspected: True

▼ 6.4 Verilog Conversion


```
In [27]: DUT.convert()
VerilogTextReader('BufferGate');
```

```
***Verilog modular from BufferGate.v***
```

```
// File: BufferGate.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:43:49 2018
```

```
`timescale 1ns/10ps
```

```
module BufferGate (
    X,
    Y
);
// Buffer Gate demo module
// Input:
//   X(bool): Input connection to wire between `X` and `Y`
// Output:
//   Y(bool): Output connection to wire between 'X' and 'Y'
```

```
input X;
output Y;
wire Y;
```

```
assign Y = X;
```

```
endmodule
```

 


Figure 8: BufferGate RTL schematic; Xilinx Vivado 2017.4


 


Figure 9: BufferGate Synthesized Schematic; Xilinx Vivado 2017.4

 

▼ 6.5 myHDL to Verilog Testbench

```
In [28]: ▼ #create BitVector for BufferGate_TBV  
          XTVs=intbv(int(''.join(XTVs.astype(str)), 2))[TestLen:]  
          XTVs, bin(XTVs)
```

```
Out[28]: (intbv(876), '1101101100')
```

```

In [29]: ▼ #Convertible testbenchs must be treated as a module
          ▼ @block
          ▼ def BufferGate_TBV():
              """
              myHDL -> Verilog testbench for module `BufferGate`
              """
              #create the signals to bind to the DUT
              X=Signal(bool(0))
              Y=Signal(bool(0))

              #print out the waveform of `X` and `Y`
              @always_comb
              def print_data():
                  print(X, Y)

              #create a register to hold the testdata vector
              #Test Signal Bit Vector
              XTV=Signal(XTVs)

              #create an instance of the `BufferGate` and
              #bind X and Y to it
              DUT=BufferGate(X, Y)

              #create the stimules action
              @instance
              def stimules():
                  for i in range(TestLen):
                      #assign X the next bit from XTV testvector reg
                      X.next=XTV[i]
                      #delay one of the smallest time intervals
                      yield delay(1)

                      #raise the stop simulation flag
                      raise StopSimulation()

              #return all internals of the Testbench
              return instances()

              #create instance of the Testbench
              TB=BufferGate_TBV()
              #run the conversion to Verilog and insure that
              #all Signal values are at there default value
              TB.convert(hdl="Verilog", initial_values=True)
              #read back the testbench into python
              VerilogTextReader('BufferGate_TBV');

```

```

<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modual from BufferGate_TBV.v***

```

```

// File: BufferGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep 3 14:43:59 2018

```

```

module BufferGate_TBV (
);
// myHDL -> Verilog testbench for module `BufferGate`

wire Y;
reg X = 0;
wire [9:0] XTV;

assign XTV = 10'd876;

always @(X, Y) begin: BUFFERGATE_TBV_PRINT_DATA
    $write("%h", X);
    $write(" ");
    $write("%h", Y);
    $write("\n");
end

assign Y = X;

initial begin: BUFFERGATE_TBV_STIMULES
    integer i;
    for (i=0; i<10; i=i+1) begin
        X <= XTV[i];
        # 1;
    end
    $finish;
end

endmodule

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_toVerilog.py:349: ToVerilogWarning: Signal is not driven: XTV
category=ToVerilogWarning

```

▼ 6.6 PYNQ-Z1 Deployment

▼ 6.6.1 Board Circuit

```

In [30]: d=schem.Drawing(unit=.5)
#add switch
SW0=d.add(e.SWITCH_SPDT2, reverse=True, label='SW0')

#connect to buffer
d.add(e.LINE, d='right', xy=SW0.a, l=d.unit*2, label='X')
d.add(e.DOT)
B0=d.add(l.BUF, label='BUF')


#buffer to LED
d.add(e.DOT)
d.add(e.LINE, d='right', l=d.unit*2, label='Y')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.LED, rglabel='LD0', d='down')

#LED to ground
d.add(e.LINE, d='down', l=d.unit*1.5)
d.add(e.GND)

#switch bottom to ground
d.add(e.LINE, d='down', xy=SW0.c, l=d.unit*4)
d.add(e.GND)

#switch top to rail
d.add(e.LINE, d='up', xy=SW0.b, l=d.unit*2.3)
d.add(e.VDD)
d.draw()

```

 

▼ 6.6.2 Board Constraint File

```
In [31]: ConstraintXDCTextReader('PYNQ_Z1Constraints_BufferGate');

***Constraint file from PYNQ_Z1Constraints_BufferGate.xdc***

## PYNQ-Z1 Board Constraints for BufferGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switch 0
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```


▼ 6.6.3 Video of Deployment

BUFFER Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=v5q5OC0SwB4\)](https://www.youtube.com/watch?v=v5q5OC0SwB4))

▼ 7 NOT

Definition 4 A NOT Gate, also called an Inverter, is a logic gate that produces the negated value of the input. Its boolean expression is typically $Y = \overline{X}$ using the overhead bar negation notation.
 
```
In [32]: d = schem.Drawing(unit=.5)
d.add(e.DOT_OPEN, l=d.unit*3, lftlabel='$X$')
d.add(l.NOT, label='$NOT$')
d.add(e.LINE)
d.add(e.DOT_OPEN, rgtlabel='$Y$')
d.draw()
```



▼ 7.1 Sympy Expression

```
In [33]: X, Y=symbols('X, Y')
        YEq=Eq(Y, ~X); YEq
```

```
Out[33]:
```

$$Y = \neg X$$

```
In [34]: TruthTabelGenrator(YEq)
```

```
Out[34]:
```

	X	Y
0	0	1
1	1	0

```
In [35]: YEqN=lambdify(X, YEq.rhs, dummify=False)
        YEqN(0), YEqN(1)
```

```
Out[35]: (True, False)
```

▼ 7.2 myHDL Module

```
In [36]: @block
        ▼ def NotGate(X, Y):
            """
            NOT gate exsample module

            Input:
                X(bool): input

            Output:
                Y(bool): ouput

            """
            ▼ @always_comb
                def logic():
                    Y.next=not X

            return instances()
```

▼ 7.3 myHDL Testing

```
In [37]: ▼ #generate random test values for NotGate_TB
        #stimules input In
        TestLen=10
        np.random.seed(14)
        XTVs=np.random.randint(0,2, TestLen).astype(int)
        XTVs
```

```
Out[37]: array([1, 0, 0, 0, 1, 1, 0, 0, 0, 0])
```

```

In [38]:
Peeker.clear()
X=Signal(bool(0)); Peeker(X, 'X')
Y=Signal(bool(0)); Peeker(Y, 'Y')

DUT=NotGate(X, Y)

▼ def NotGate_TB():
    """
    myHDL only testbench for module `NotGate`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            X.next=int(XTVs[i])
            yield delay(1)

            raise StopSimulation()

    return instances()

sim=Simulation(DUT, NotGate_TB(), *Peeker.instances()).run()

```

```

In [39]:
Peeker.to_wavedrom()

```

```

In [40]:
NotData=Peeker.to_dataframe()
NotData

```

```

Out[40]:
   X  Y
0  1  0
1  0  1
4  1  0
6  0  1

```

```

In [41]:
NotData['YRef']=NotData['X'].apply(YEqN).astype(int)
NotData

```

```

Out[41]:
   X  Y  YRef
0  1  0     0
1  0  1     1
4  1  0     0
6  0  1     1

```

```

In [42]:
Test=(NotData['Y']==NotData['YRef']).all()
print(f'Module `NotGate` works as expected: {Test}')

```

Module `NotGate` works as expected: True

▼ 7.4 Verilog Conversion

```
In [43]: DUT.convert()
VerilogTextReader('NotGate');

***Verilog modular from NotGate.v***

// File: NotGate.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:44:38 2018

`timescale 1ns/10ps

module NotGate (
    X,
    Y
);
// NOT gate exsample module
//
// Input:
//     X(bool): input
//
// Output:
//     Y(bool): ouput

input X;
output Y;
wire Y;

assign Y = (!X);

endmodule
```


 


Figure 11: NotGate RTL schematic; Xilinx Vivado 2017.4

 

Processing math: 100%

Figure 12: NotGate Synthesized Schematic; Xilinx Vivado 2017.4

 


Figure 13: NotGate Implemented Schematic; Xilinx Vivado 2017.4

▼ 7.5 myHDL to Verilog Testbench

```
In [44]: ▼ #create BitVector for NotGate_TBV
          XTVs=intbv(int(''.join(XTVs.astype(str)), 2))[TestLen:]
          XTVs, bin(XTVs)
```

```
Out[44]: (intbv(560), '1000110000')
```

```
In [45]: @block
def NotGate_TBV():
    """
    myHDL -> Verilog testbench for module `NotGate`
    """
    X=Signal(bool(0))
    Y=Signal(bool(0))

    @always_comb
    def print_data():
        print(X, Y)

    #Test Signal Bit Vector
    XTV=Signal(XTVs)

    DUT=NotGate(X, Y)

    @instance
    def stimules():
        for i in range(TestLen):
            X.next=XTV[i]
            yield delay(1)

        raise StopSimulation()
    return instances()

TB=NotGate_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('NotGate_TBV');
```

```
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from NotGate_TBV.v***
```

```
// File: NotGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:44:48 2018
```

```
`timescale 1ns/10ps

module NotGate_TBV (

);
// myHDL -> Verilog testbench for module `NotGate`
```

```
wire Y;
reg X = 0;
wire [9:0] XTV;

assign XTV = 10'd560;
```

```
Processing math: 100% always @(X, Y) begin: NOTGATE_TBV_PRINT_DATA
    $write("%h", X);
```

```
        $write(" ");
        $write("%h", Y);
        $write("\n");
    end
```

```
assign Y = (!X);
```

```
initial begin: NOTGATE_TBV_STIMULES
    integer i;
    for (i=0; i<10; i=i+1) begin
        X <= XTV[i];
        # 1;
    end
    $finish;
end

endmodule
```

```
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: XTV
  category=ToVerilogWarning
```

▼ 7.6 PYNQ-Z1 Deployment

▼ 7.6.1 Board Circuit

```

In [46]: d=schem.Drawing(unit=.5)
#add switch
SW0=d.add(e.SWITCH_SPDT2, reverse=True, label='SW0')

#connect to buffer
d.add(e.LINE, d='right', xy=SW0.a, l=d.unit*2, label='X')
d.add(e.DOT)
N0=d.add(l.NOT, label='NOT')


#buffer to LED
d.add(e.DOT)
d.add(e.LINE, d='right', l=d.unit*2, label='Y')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.LED, rgtlabel='LD0', d='down')

#LED to ground
d.add(e.LINE, d='down', l=d.unit*1.5)
d.add(e.GND)

#switch bottom to ground
d.add(e.LINE, d='down', xy=SW0.c, l=d.unit*4)
d.add(e.GND)

#switch top to rail
d.add(e.LINE, d='up', xy=SW0.b, l=d.unit*2.3)
d.add(e.VDD)
d.draw()

```

 

▼ 7.6.2 Board Constraint

```
In [47]: ConstraintXDCTextReader('PYNQ_Z1Constraints_NotGate');

***Constraint file from PYNQ_Z1Constraints_NotGate.xdc***

## PYNQ-Z1 Board Constraints for NotGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switch 0
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```

▼ 7.6.3 Video of Deployment

NOT Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=5II5zOh6XAU\)](https://www.youtube.com/watch?v=5II5zOh6XAU))

▼ 8 AND

Definition 5 An AND Gate is a logic gate the will yield a True response if and only if all of its inputs are also True. Its boolean expression is typically $Y = X_0 \cdot X_1$ using the multiplicative dot notation. Since if True is mapped to 1 and False is mapped 0, its output behavior is like that of multiplication of 1 and 0

```
In [48]: d = schem.Drawing(unit=.5)
G = d.add(l.AND2, label='$AND_2$')
d.add(e.DOT_OPEN, xy=G.out, rgtlabel='$Y$')
d.add(e.DOT_OPEN, xy=G.in1, lftlabel='$X_1$')
d.add(e.DOT_OPEN, xy=G.in2, lftlabel='$X_0$')
d.draw()
```

AND₂



▼ 8.1 Sympy Expression

```
In [49]: X0, X1, Y=symbols('X_0, X_1, Y')
        YEq=Eq(Y, X0&X1); YEq
```

Out[49]:
$$Y = X_0 \wedge X_1$$

```
In [50]: TruthTabelGenrator(YEq)
```

Out[50]:

	x_0	x_1	Y
0	0	0	0
1	0	1	0
2	1	0	0
3	1	1	1

```
In [51]: YEqN=lambdify([X0, X1], YEq.rhs, dummify=False)
        SystmaticVals=np.array(list(itertools.product([0,1], repeat=2)))
        SystmaticVals, YEqN(SystmaticVals[:, 1], SystmaticVals[:, 0]).astype(ir
```

Out[51]: (array([[0, 0],
[0, 1],
[1, 0],
[1, 1]]), array([0, 0, 0, 1]))

▼ 8.2 myHDL Module

```
In [52]: @block
def AndGate(X0, X1, Y):
    """
    And Gate demo module

    Input:
        X0(bool): And gate input 0
        X1(bool): And gate input 1

    Output:
        Y(bool): And gate output

    """
    @always_comb
    def logic():
        #note here that `and` is used since this
        #is a bit wise AND
        Y.next=X0 and X1

        #if `&` had been used the conversion
        #would yield `&` the .all() AND
        # when dealing with bus's and behavior mux's this
        #distiction must be known
        #see:
        # https://stackoverflow.com/questions/17327680/what-is-the-dif

    return instances()
```

▼ 8.3 myHDL Testing

```
In [53]: #generate systmatic and random test values for AndGate_TB
#stimules inputs X1 and X2
TestLen=10
SystmaticVals=list(itertools.product([0,1], repeat=2))
X0TVs=np.array([i[1] for i in SystmaticVals]).astype(int)
np.random.seed(15)
X0TVs=np.append(X0TVs, np.random.randint(0,2, TestLen)).astype(int)

X1TVs=np.array([i[0] for i in SystmaticVals]).astype(int)
#the random genrator must have a differint seed between each generation
#call in order to produce differint values for each call
np.random.seed(16)
X1TVs=np.append(X1TVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(X1TVs)
SystmaticVals, X1TVs, X0TVs, TestLen
```

```
Out[53]: ((0, 0), (0, 1), (1, 0), (1, 1)),
array([0, 0, 1, 1, 1, 0, 1, 1, 1, 1, 0, 1, 1, 0]),
array([0, 1, 0, 1, 0, 1, 0, 1, 1, 0, 0, 1, 1, 1]),
14)
```



```

In [54]:
Peeker.clear()
X0=Signal(bool(0)); Peeker(X0, 'X0')
X1=Signal(bool(0)); Peeker(X1, 'X1')
Y=Signal(bool(0)); Peeker(Y, 'Y')

DUT=AndGate(X0, X1, Y)

▼ def AndGate_TB():
    """
    myHDL only testbench for module `AndGate`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            X0.next=int(X0TVs[i])
            X1.next=int(X1TVs[i])
            yield delay(1)

            raise StopSimulation()

        return instances()

sim=Simulation(DUT, AndGate_TB(), *Peeker.instances()).run()

```

```

In [55]:
Peeker.to_wavedrom('X1', 'X0', 'Y')

```

```

In [56]:
AndData=Peeker.to_dataframe()
AndData=AndData[['X1', 'X0', 'Y']]
AndData

```

```

Out[56]:

```

	X1	X0	Y
0	0	0	0
1	0	1	0
2	1	0	0
3	1	1	1
4	1	0	0
5	0	1	0
6	1	0	0
7	1	1	1
9	1	0	0
10	0	0	0
11	1	1	1
13	0	1	0

```
In [57]: AndData['YRef']=AndData.apply(lambda row:YEqN(row['X0'], row['X1']), axis=1)
AndData
```

```
Out[57]:
```

	X1	X0	Y	YRef
0	0	0	0	0
1	0	1	0	0
2	1	0	0	0
3	1	1	1	1
4	1	0	0	0
5	0	1	0	0
6	1	0	0	0
7	1	1	1	1
9	1	0	0	0
10	0	0	0	0
11	1	1	1	1
13	0	1	0	0

```
In [58]: Test=(AndData['Y']==AndData['YRef']).all()
print(f'Module `AndGate` works as expected: {Test}')
```

Module `AndGate` works as expected: True

▼ 8.4 Verilog Conversion

```
In [59]: DUT.convert()  
VerilogTextReader('AndGate');
```

```
***Verilog modular from AndGate.v***
```

```
// File: AndGate.v  
// Generated by MyHDL 0.10  
// Date: Mon Sep  3 14:45:30 2018
```

```
`timescale 1ns/10ps
```

```
module AndGate (  
    X0,  
    X1,  
    Y  
);  
// And Gate demo module  
//  
// Input:  
//    X0(bool): And gate input 0  
//    X1(bool): And gate input 1  
//  
// Output:  
//    Y(bool): And gate output
```

```
input X0;  
input X1;  
output Y;  
wire Y;
```

```
assign Y = (X0 && X1);
```

```
endmodule
```

 


Figure 14: AndGate RTL schematic; Xilinx Vivado 2017.4

 


Figure 15: AndGate Synthesized Schematic; Xilinx Vivado 2017.4

 


Figure 16: AndGate Implemented Schematic; Xilinx Vivado 2017.4

▼ 8.5 myHDL to Verilog Testbench

```
In [60]: ▼ #create BitVector for AndGate_TBV
X0TVs=intbv(int(''.join(X0TVs.astype(str)), 2))[TestLen:]
X1TVs=intbv(int(''.join(X1TVs.astype(str)), 2))[TestLen:]
X0TVs, bin(X0TVs), X1TVs, bin(X1TVs)
```

```
Out[60]: (intbv(5479), '1010101100111', intbv(3830), '111011110110')
```

```
In [61]: @block
def AndGate_TBV():
    """
    myHDL -> Verilog testbench for module `AndGate`
    """
    X0=Signal(bool(0))
    X1=Signal(bool(0))
    Y=Signal(bool(0))

    @always_comb
    def print_data():
        print(X0, X1, Y)

    #Test Signal Bit Vectors
    X0TV=Signal(X0TVs)
    X1TV=Signal(X1TVs)

    DUT=AndGate(X0, X1, Y)

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TV[i])
            X1.next=int(X1TV[i])
            yield delay(1)

        raise StopSimulation()
    return instances()

TB=AndGate_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('AndGate_TBV');
```

```
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from AndGate_TBV.v***
```

```
// File: AndGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:45:40 2018
```

```
`timescale 1ns/10ps
```

```
module AndGate_TBV (
```

```
);
// myHDL -> Verilog testbench for module `AndGate`
```

```
wire Y;
reg X0 = 0;
reg X1 = 0;
wire [13:0] X0TV;
wire [13:0] X1TV;
```

```
assign X0TV = 14'd5479;
assign X1TV = 14'd3830;
```

```
always @(X1, Y, X0) begin: ANDGATE_TBV_PRINT_DATA
    $write("%h", X0);
    $write(" ");
    $write("%h", X1);
    $write(" ");
    $write("%h", Y);
    $write("\n");
end
```

```
assign Y = (X0 && X1);
```

```
initial begin: ANDGATE_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        X0 <= X0TV[i];
        X1 <= X1TV[i];
        # 1;
    end
    $finish;
end

endmodule
```

```
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X0TV
    category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X1TV
    category=ToVerilogWarning
```

▼ 8.6 PYNQ-Z1 Deployment

▼ 8.6.1 Board Circuit

```

In [62]: d=schem.Drawing(unit=.5)
#add elements
G=d.add(l.AND2,d='right', label='$AND_2$')


#Gate to led to gnd

d.add(e.LINE, d='right', xy=G.out)
d.add(e.DOT, label='$Y$')
d.add(e.LINE, d='down', l=d.unit*2)
LD0=d.add(e.LED, d='down', label='LD0')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.GND)

d.add(e.LINE, d='left', xy=G.in1, l=d.unit)
d.add(e.DOT, label='$X_0$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='up', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*2)
SW0=d.add(e.SWITCH_SPDT, lftlabel='SW0')
d.add(e.GND, xy=SW0.c)
d.add(e.VDD, xy=SW0.b)

d.add(e.LINE, d='left', xy=G.in2, l=d.unit)
d.add(e.DOT, botlabel='$X_1$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='down', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*4)
SW1=d.add(e.SWITCH_SPDT, lftlabel='SW1')
d.add(e.GND, xy=SW1.c)
d.add(e.VDD, xy=SW1.b)
d.draw()

```

 

▼ 8.6.2 Board Constraint

```
In [63]: ConstraintXDCTextReader('PYNQ_Z1Constraints_AndGate');

***Constraint file from PYNQ_Z1Constraints_AndGate.xdc***

## PYNQ-Z1 Board Constraints for AndGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switchs 0,1
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X0}]
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {X1}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```


▼ 8.6.3 Video of Deployment

AND Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=PqLGQezfr4U\)](https://www.youtube.com/watch?v=PqLGQezfr4U))

▼ 9 OR

Definition 6 An OR Gate is a logic gate that will yield a True response if any of its inputs are True. Its boolean expression is typically $Y = X_0 + X_1$ using the addition notation. Since if True is mapped to 1 and False is mapped to 0, its output behavior is like that of the addition of 1 and 0 with the constraint of $1+1=1$ which is an axiom of Boolean Algebra.
 
```
In [64]: d = schem.Drawing(unit=.5)
G = d.add(l.AND2, label='OR_2$')
d.add(e.DOT_OPEN, xy=G.out, rgtlabel='$Y$')
d.add(e.DOT_OPEN, xy=G.in1, lftlabel='$X_1$')
d.add(e.DOT_OPEN, xy=G.in2, lftlabel='$X_0$')
d.draw()
```



▼ 9.1 Sympy Expression


```
In [65]: X0, X1, Y=symbols('X_0, X_1, Y')
        YEq=Eq(Y, X0|X1); YEq
```

Out[65]:
$$Y = X_0 \vee X_1$$

```
In [66]: TruthTabelGenrator(YEq)
```

Out[66]:

	x_0	x_1	Y
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

```
In [67]: YEqN=lambdify([X0, X1], YEq.rhs, dummify=False)
        SystmaticVals=np.array(list(itertools.product([0,1], repeat=2)))
        SystmaticVals, YEqN(SystmaticVals[:, 1], SystmaticVals[:, 0]).astype(ir
```

Out[67]: (array([[0, 0],
[0, 1],
[1, 0],
[1, 1]]), array([0, 1, 1, 1]))

▼ 9.2 myHDL Module

```
In [68]: @block
def OrGate(X0, X1, Y):
    """
    Or Gate demo module

    Input:
        X0(bool): Or gate input 0
        X1(bool): Or gate input 1

    Output:
        Y(bool): Or gate output

    """
    @always_comb
    def logic():
        #note here that `or` is used since this
        #is a bit wise OR
        Y.next=X0 or X1

        #if `|` had been used the conversion
        #would yield `||` the .all() OR
        # when dealing with bus's and behavior mux's this
        #distiction must be known
        #see:
        # https://stackoverflow.com/questions/17327680/what-is-the-dif

    return instances()
```

▼ 9.3 myHDL Testing

```
In [69]: #generate systmatic and random test values for OrGate_TB
#stimules inputs X1 and X2
TestLen=10
SystematicVals=list(itertools.product([0,1], repeat=2))
X0TVs=np.array([i[1] for i in SystematicVals]).astype(int)
np.random.seed(17)
X0TVs=np.append(X0TVs, np.random.randint(0,2, TestLen)).astype(int)

X1TVs=np.array([i[0] for i in SystematicVals]).astype(int)
np.random.seed(18)
X1TVs=np.append(X1TVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(X1TVs)
SystematicVals, X1TVs, X0TVs, TestLen
```

```
Out[69]: ((0, 0), (0, 1), (1, 0), (1, 1)),
array([0, 0, 1, 1, 0, 1, 0, 1, 0, 1, 0, 0, 0, 0]),
array([0, 1, 0, 1, 1, 1, 1, 0, 0, 1, 0, 1, 0, 1]),
14)
```

```

In [70]:
Peeker.clear()
X0=Signal(bool(0)); Peeker(X0, 'X0')
X1=Signal(bool(0)); Peeker(X1, 'X1')
Y=Signal(bool(0)); Peeker(Y, 'Y')

DUT=OrGate(X0, X1, Y)

▼ def OrGate_TB():
    """
    myHDL only testbench for module `OrGate`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            X0.next=int(X0TVs[i])
            X1.next=int(X1TVs[i])
            yield delay(1)

            raise StopSimulation()

        return instances()

sim=Simulation(DUT, OrGate_TB(), *Peeker.instances()).run()

```

```

In [71]: Peeker.to_wavedrom('X1', 'X0', 'Y')

```

```
In [72]: OrData=Peeker.to_dataframe()  
OrData=OrData[['X1', 'X0', 'Y']]  
OrData
```

Out[72]:

	X1	X0	Y
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1
4	0	1	1
5	1	1	1
6	0	1	1
7	1	0	1
8	0	0	0
9	1	1	1
10	0	0	0
11	0	1	1
12	0	0	0
13	0	1	1

```
In [73]: OrData['YRef']=OrData.apply(lambda row:YEqN(row['X0'], row['X1']), axis  
OrData
```

Out[73]:

	X1	X0	Y	YRef
0	0	0	0	0
1	0	1	1	1
2	1	0	1	1
3	1	1	1	1
4	0	1	1	1
5	1	1	1	1
6	0	1	1	1
7	1	0	1	1
8	0	0	0	0
9	1	1	1	1
10	0	0	0	0
11	0	1	1	1
12	0	0	0	0
13	0	1	1	1

```
In [74]: Test=(OrData['Y']==OrData['YRef']).all()  
print(f'Module `OrGate` works as expected: {Test}')
```

Module `OrGate` works as expected: True

▼ 9.4 Verilog Conversion

```
In [75]: DUT.convert()  
VerilogTextReader('OrGate');  
  
***Verilog modular from OrGate.v***
```

```
// File: OrGate.v  
// Generated by MyHDL 0.10  
// Date: Mon Sep  3 14:46:15 2018
```


```
`timescale 1ns/10ps
```

```
module OrGate (  
    X0,  
    X1,  
    Y  
);  
// Or Gate demo module  
//  
// Input:  
//    X0(bool): Or gate input 0  
//    X1(bool): Or gate input 1  
//  
// Output:  
//    Y(bool): Or gate output
```

```
input X0;  
input X1;  
output Y;  
wire Y;
```

```
assign Y = (X0 || X1);
```

```
endmodule
```

 

Processing math: 100%

Figure 17: OrGate RTL schematic; Xilinx Vivado 2017.4

 


Figure 18: OrGate Synthesized Schematic; Xilinx Vivado 2017.4

 


Figure 19: OrGate Implemented Schematic; Xilinx Vivado 2017.4

▼ 9.5 myHDL to Verilog Testbench

```
In [76]: ▼ #create BitVector for OrGate_TBV
X0TVs=intbv(int(''.join(X0TVs.astype(str)), 2))[TestLen:]
X1TVs=intbv(int(''.join(X1TVs.astype(str)), 2))[TestLen:]
X0TVs, bin(X0TVs), X1TVs, bin(X1TVs)
```

```
Out[76]: (intbv(6037), '1011110010101', intbv(3408), '110101010000')
```

```
In [77]: @block
def OrGate_TBV():
    """
    myHDL -> Verilog testbench for module `OrGate`
    """
    X0=Signal(bool(0))
    X1=Signal(bool(0))
    Y=Signal(bool(0))

    @always_comb
    def print_data():
        print(X0, X1, Y)

    #Test Signal Bit Vectors
    X0TV=Signal(X0TVs)
    X1TV=Signal(X1TVs)

    DUT=OrGate(X0, X1, Y)

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TV[i])
            X1.next=int(X1TV[i])
            yield delay(1)

        raise StopSimulation()
    return instances()

TB=OrGate_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('OrGate_TBV');
```

```
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modulal from OrGate_TBV.v***
```

```
// File: OrGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:46:26 2018
```

```
`timescale 1ns/10ps
```

```
module OrGate_TBV (
```

```
);
// myHDL -> Verilog testbench for module `OrGate`
```

```
wire Y;
reg X0 = 0;
reg X1 = 0;
wire [13:0] X0TV;
wire [13:0] X1TV;
```

```

assign X0TV = 14'd6037;
assign X1TV = 14'd3408;

always @(X1, Y, X0) begin: ORGATE_TBV_PRINT_DATA
    $write("%h", X0);
    $write(" ");
    $write("%h", X1);
    $write(" ");
    $write("%h", Y);
    $write("\n");
end

assign Y = (X0 || X1);

initial begin: ORGATE_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        X0 <= X0TV[i];
        X1 <= X1TV[i];
        # 1;
    end
    $finish;
end

endmodule

```

```

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X0TV
    category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X1TV
    category=ToVerilogWarning

```

▼ 9.6 PYNQ-Z1 Deployment

▼ 9.6.1 Board Circuit


```

In [78]: d=schem.Drawing(unit=.5)
#add elements
G=d.add(l.OR2,d='right', label='$OR_2$')


#Gate to led to gnd

d.add(e.LINE, d='right', xy=G.out)
d.add(e.DOT, label='$Y$')
d.add(e.LINE, d='down', l=d.unit*2)
LD0=d.add(e.LED, d='down', label='LD0')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.GND)

d.add(e.LINE, d='left', xy=G.in1, l=d.unit)
d.add(e.DOT, label='$X_0$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='up', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*2)
SW0=d.add(e.SWITCH_SPDT, lftlabel='SW0')
d.add(e.GND, xy=SW0.c)
d.add(e.VDD, xy=SW0.b)

d.add(e.LINE, d='left', xy=G.in2, l=d.unit)
d.add(e.DOT, botlabel='$X_1$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='down', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*4)
SW1=d.add(e.SWITCH_SPDT, lftlabel='SW1')
d.add(e.GND, xy=SW1.c)
d.add(e.VDD, xy=SW1.b)
d.draw()

```

 

▼ 9.6.2 Board Constraint

```
In [79]: ConstraintXDCTextReader('PYNQ_Z1Constraints_OrGate');

***Constraint file from PYNQ_Z1Constraints_OrGate.xdc***

## PYNQ-Z1 Board Constraints for XorGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switchs 0,1
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X0}]
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {X1}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```


▼ 9.6.3 Video of Deployment

OR Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=QKhMft17sac\)](https://www.youtube.com/watch?v=QKhMft17sac))

▼ 10 XOR

Definition 7 An XOR Gate is a logic gate the will yield a True response if an only if only one of its inputs are True. Its boolean expression is typically $Y = X_0 \oplus X_1$ using its typical notation, wich is a refinement of the $+$ notation used for an OR Gate. But can also be expressed as $Y = X_0 \overline{X_1} + \overline{X_0} X_1 = (X_0 + X_1) \cdot (\overline{X_0} + \overline{X_1})$
 
```
In [80]: d = schem.Drawing(unit=.5)
G = d.add(1.XOR2, label='$XOR_2$')
d.add(e.DOT_OPEN, xy=G.out, rgtlabel='$Y$')
d.add(e.DOT_OPEN, xy=G.in1, lftlabel='$X_1$')
d.add(e.DOT_OPEN, xy=G.in2, lftlabel='$X_0$')
d.draw()
```



▼ 10.1 Sympy Expression

```
In [81]: X0, X1, Y=symbols('X_0, X_1, Y')
        YEq=Eq(Y, X0^X1); YEq
```

```
Out[81]:
```

$$Y = X_0 \vee X_1$$

```
In [82]: TruthTabelGenrator(YEq)
```

```
Out[82]:
```

	X_0	X_1	Y
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	0

```
In [83]: #lampdfy must have maping manully set from `Xor` to `np.bitwise_xor`
        YEqN=lambdify([X0, X1], YEq.rhs, {'Xor':np.bitwise_xor}, dummify=False)
        SystmaticVals=np.array(list(itertools.product([0,1], repeat=2)))
        SystmaticVals, YEqN(SystmaticVals[:, 1], SystmaticVals[:, 0]).astype(ir
```

```
Out[83]: (array([[0, 0],
                  [0, 1],
                  [1, 0],
                  [1, 1]]), array([0, 1, 1, 0]))
```

▼ 10.2 myHDL Module

```
In [84]: @block
        def XorGate(X0, X1, Y):
            """
            XOR Gate demo module

            Input:
            X0(bool): XOR gate input 0
            X1(bool): XOR gate input 1

            Output:
            Y(bool): XOR gate ouput

            """
            @always_comb
            def logic():
                Y.next=X0 ^ X1

            return instances()
```

▼ 10.3 myHDL Testing

```
In [85]: #generate systmatic and random test values for XorGate_TB
#stimules inputs X1 and X2
TestLen=10
SystematicVals=list(itertools.product([0,1], repeat=2))
X0TVs=np.array([i[1] for i in SystematicVals]).astype(int)
np.random.seed(19)
X0TVs=np.append(X0TVs, np.random.randint(0,2, TestLen)).astype(int)

X1TVs=np.array([i[0] for i in SystematicVals]).astype(int)
np.random.seed(20)
X1TVs=np.append(X1TVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(X1TVs)
SystematicVals, X1TVs, X0TVs, TestLen
```

```
Out[85]: [(0, 0), (0, 1), (1, 0), (1, 1)],
array([0, 0, 1, 1, 1, 0, 1, 1, 0, 0, 1, 0, 1, 0]),
array([0, 1, 0, 1, 1, 0, 1, 0, 0, 1, 0, 0, 1, 0]),
14)
```

```
In [86]: Peeker.clear()
X0=Signal(bool(0)); Peeker(X0, 'X0')
X1=Signal(bool(0)); Peeker(X1, 'X1')
Y=Signal(bool(0)); Peeker(Y, 'Y')

DUT=XorGate(X0, X1, Y)

def XorGate_TB():
    """
    myHDL only testbench for module `XorGate`
    """

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TVs[i])
            X1.next=int(X1TVs[i])
            yield delay(1)

        raise StopSimulation()

    return instances()

sim=Simulation(DUT, XorGate_TB(), *Peeker.instances()).run()
```

```
In [87]: Peeker.to_wavedrom('X1', 'X0', 'Y')
```

```
In [88]: XorData=Peeker.to_dataframe()  
XorData=XorData[['X1', 'X0', 'Y']]  
XorData
```

```
Out[88]:
```

	X1	X0	Y
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	0
5	0	0	0
6	1	1	0
7	1	0	1
8	0	0	0
9	0	1	1
10	1	0	1
11	0	0	0
12	1	1	0
13	0	0	0

```
In [89]: XorData['YRef']=XorData.apply(lambda row:YEqN(row['X0'], row['X1']), axis=1)  
XorData
```

```
Out[89]:
```

	X1	X0	Y	YRef
0	0	0	0	0
1	0	1	1	1
2	1	0	1	1
3	1	1	0	0
5	0	0	0	0
6	1	1	0	0
7	1	0	1	1
8	0	0	0	0
9	0	1	1	1
10	1	0	1	1
11	0	0	0	0
12	1	1	0	0
13	0	0	0	0

```
In [90]: Test=(XorData['Y']==XorData['YRef']).all()  
print(f'Module `XorGate` works as expected: {Test}')
```

Module `XorGate` works as expected: True

▼ 10.4 Verilog Conversion

```
In [91]: DUT.convert()  
VerilogTextReader('XorGate');  
  
***Verilog modular from XorGate.v***
```

```
// File: XorGate.v  
// Generated by MyHDL 0.10  
// Date: Mon Sep  3 14:48:12 2018
```

```
`timescale 1ns/10ps
```

```
module XorGate (  
    X0,  
    X1,  
    Y  
);  
// XOR Gate demo module  
//  
// Input:  
//    X0(bool): XOR gate input 0  
//    X1(bool): XOR gate input 1  
//  
// Output:  
//    Y(bool): XOR gate output
```

```
input X0;  
input X1;  
output Y;  
wire Y;
```

```
assign Y = (X0 ^ X1);
```

```
endmodule
```

 


Figure 20: XorGate RTL schematic; Xilinx Vivado 2017.4

 


Figure 21: XorGate Synthesized Schematic; Xilinx Vivado 2017.4

 


Figure 22: XorGate Implemented Schematic; Xilinx Vivado 2017.4

▼ 10.5 myHDL to Verilog Testbench

```
In [92]: ▼ #create BitVector for XorGate_TBV
X0TVs=intbv(int(''.join(X0TVs.astype(str)), 2))[TestLen:]
X1TVs=intbv(int(''.join(X1TVs.astype(str)), 2))[TestLen:]
X0TVs, bin(X0TVs), X1TVs, bin(X1TVs)
```

```
Out[92]: (intbv(5778), '1011010010010', intbv(3786), '111011001010')
```

```
In [93]: @block
def XorGate_TBV():
    """
    myHDL -> Verilog testbench for module `XorGate`
    """
    X0=Signal(bool(0))
    X1=Signal(bool(0))
    Y=Signal(bool(0))

    @always_comb
    def print_data():
        print(X0, X1, Y)

    #Test Signal Bit Vectors
    X0TV=Signal(X0TVs)
    X1TV=Signal(X1TVs)

    DUT=XorGate(X0, X1, Y)

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TV[i])
            X1.next=int(X1TV[i])
            yield delay(1)

        raise StopSimulation()
    return instances()

TB=XorGate_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('XorGate_TBV');
```

```
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from XorGate_TBV.v***
```

```
// File: XorGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:48:26 2018
```

```
`timescale 1ns/10ps
```

```
module XorGate_TBV (
```

```
);
// myHDL -> Verilog testbench for module `XorGate`
```

```
wire Y;
reg X0 = 0;
reg X1 = 0;
wire [13:0] X0TV;
wire [13:0] X1TV;
```



```
assign X0TV = 14'd5778;
assign X1TV = 14'd3786;
```

```
always @(X1, Y, X0) begin: XORGATE_TBV_PRINT_DATA
    $write("%h", X0);
    $write(" ");
    $write("%h", X1);
    $write(" ");
    $write("%h", Y);
    $write("\n");
end
```

```
assign Y = (X0 ^ X1);
```

```
initial begin: XORGATE_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        X0 <= X0TV[i];
        X1 <= X1TV[i];
        # 1;
    end
    $finish;
end

endmodule
```

```
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X0TV
  category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X1TV
  category=ToVerilogWarning
```

▼ 10.6 PYNQ-Z1 Deployment

▼ 10.6.1 Board Circuit

```

In [94]: d=schem.Drawing(unit=.5)
#add elements
G=d.add(l.XOR2,d='right', label='$XOR_2$')


#Gate to led to gnd

d.add(e.LINE, d='right', xy=G.out)
d.add(e.DOT, label='$Y$')
d.add(e.LINE, d='down', l=d.unit*2)
LD0=d.add(e.LED, d='down', label='LD0')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.GND)

d.add(e.LINE, d='left', xy=G.in1, l=d.unit)
d.add(e.DOT, label='$X_0$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='up', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*2)
SW0=d.add(e.SWITCH_SPDT, lftlabel='SW0')
d.add(e.GND, xy=SW0.c)
d.add(e.VDD, xy=SW0.b)

d.add(e.LINE, d='left', xy=G.in2, l=d.unit)
d.add(e.DOT, botlabel='$X_1$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='down', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*4)
SW1=d.add(e.SWITCH_SPDT, lftlabel='SW1')
d.add(e.GND, xy=SW1.c)
d.add(e.VDD, xy=SW1.b)
d.draw()

```

 

▼ 10.6.2 Board Constraint

```
In [95]: ConstraintXDCTextReader('PYNQ_Z1Constraints_XorGate');

***Constraint file from PYNQ_Z1Constraints_XorGate.xdc***

## PYNQ-Z1 Board Constraints for OrGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switchs 0,1
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X0}]
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {X1}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```

▼ 10.6.3 Video of Deployment

XOR Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=Uys0Zhs7rIU\)](https://www.youtube.com/watch?v=Uys0Zhs7rIU))


▼ 11 NAND

Definition 8 A NAND Gate is the negated, or the De Morgan equivalent, of an AND Gate. Such that is output will be True whenever there are False inputs to the gate. Its boolean expression is $Y = \overline{X_0 \cdot X_1}$

One peculiar aspect of the NAND Gate is that from a pure Boolean algebra position it is one of the two "Universal Gates". Which means that any other gate can be constructed from no more than NAND Gates. See https://en.wikipedia.org/wiki/NAND_logic#Making_other_gates_by_using_NAND_gates (https://en.wikipedia.org/wiki/NAND_logic#Making_other_gates_by_using_NAND_gates) for more info. And while this somewhat holds True for ASIC circuits, this not entirely true in terms of FPGAs

```
In [96]: d = schem.Drawing(unit=.5)
G = d.add(l.NAND2, label='$NAND_2$')
d.add(e.DOT_OPEN, xy=G.out, rgtlabel='$Y$')
d.add(e.DOT_OPEN, xy=G.in1, lftlabel='$X_1$')
d.add(e.DOT_OPEN, xy=G.in2, lftlabel='$X_0$')
d.draw()
```

NAND₂

 

▼ 11.1 Sympy Expression

```
In [97]: X0, X1, Y=symbols('X_0, X_1, Y')
YEq=Eq(Y, Nand(X0,X1)); YEq
```

Out[97]:
$$Y = \neg(X_0 \wedge X_1)$$

```
In [98]: TruthTabelGenrator(YEq)
```

Out[98]:

	X_0	X_1	Y
0	0	0	1
1	0	1	1
2	1	0	1
3	1	1	0

```
In [99]: YEqN=lambdify([X0, X1], YEq.rhs, dummify=False)
SystematicVals=np.array(list(itertools.product([0,1], repeat=2)))
SystematicVals, YEqN(SystematicVals[:, 1], SystematicVals[:, 0]).astype(ir
```

Out[99]: (array([[0, 0],
[0, 1],
[1, 0],
[1, 1]]), array([1, 1, 1, 0]))

▼ 11.2 myHDL Module

```
In [100]: @block
def NAndGate(X0, X1, Y):
    """
    NAND Gate demo module

    Input:
        X0(bool): NAnd gate input 0
        X1(bool): NAnd gate input 1

    Output:
        Y(bool): NAnd gate output

    """
    @always_comb
    def logic():
        #note here that `and` is used since this
        #is a bit wise AND
        Y.next=not(X0 and X1)

        #if `&` had been used the conversion
        #would yield `&` the .all() AND
        # when dealing with bus's and behavior mux's this
        #distiction must be known
        #see:
        # https://stackoverflow.com/questions/17327680/what-is-the-dif

    return instances()
```

▼ 11.3 myHDL Testing

```
In [101]: #generate systmatic and random test values for AndGate_TB
#stimules inputs X1 and X2
TestLen=10
SystmaticVals=list(itertools.product([0,1], repeat=2))
X0TVs=np.array([i[1] for i in SystmaticVals]).astype(int)
np.random.seed(21)
X0TVs=np.append(X0TVs, np.random.randint(0,2, TestLen)).astype(int)

X1TVs=np.array([i[0] for i in SystmaticVals]).astype(int)
np.random.seed(23)
X1TVs=np.append(X1TVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(X1TVs)
SystmaticVals, X1TVs, X0TVs, TestLen
```

```
Out[101]: ((0, 0), (0, 1), (1, 0), (1, 1)),
array([0, 0, 1, 1, 1, 0, 0, 1, 0, 0, 1, 1, 0, 1]),
array([0, 1, 0, 1, 1, 1, 0, 0, 0, 0, 0, 1, 0, 0]),
14)
```

```

In [102]:
Peeker.clear()
X0=Signal(bool(0)); Peeker(X0, 'X0')
X1=Signal(bool(0)); Peeker(X1, 'X1')
Y=Signal(bool(0)); Peeker(Y, 'Y')

DUT=NAndGate(X0, X1, Y)

▼ def NAndGate_TB():
    """
    myHDL only testbench for module `NAndGate`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            X0.next=int(X0TVs[i])
            X1.next=int(X1TVs[i])
            yield delay(1)

            raise StopSimulation()

        return instances()

sim=Simulation(DUT, NAndGate_TB(), *Peeker.instances()).run()

```

```

In [103]:
Peeker.to_wavedrom('X1', 'X0', 'Y')

```

```

In [104]:
NAndData=Peeker.to_dataframe()
NAndData=NAndData[['X1', 'X0', 'Y']]
NAndData

```

```

Out[104]:

```

	X1	X0	Y
0	0	0	1
1	0	1	1
2	1	0	1
3	1	1	0
5	0	1	1
6	0	0	1
7	1	0	1
8	0	0	1
10	1	0	1
11	1	1	0
12	0	0	1
13	1	0	1

```
In [105]: NAndData['YRef']=NAndData.apply(lambda row:YEqN(row['X0'], row['X1']),  
NAndData
```

```
Out[105]:
```

	X1	X0	Y	YRef
0	0	0	1	1
1	0	1	1	1
2	1	0	1	1
3	1	1	0	0
5	0	1	1	1
6	0	0	1	1
7	1	0	1	1
8	0	0	1	1
10	1	0	1	1
11	1	1	0	0
12	0	0	1	1
13	1	0	1	1

```
In [106]: Test=(NAndData['Y']==NAndData['YRef']).all()  
print(f'Module `NAndGate` works as expected: {Test}')
```

```
Module `NAndGate` works as expected: True
```

▼ 11.4 Verilog Conversion

```
In [107]: DUT.convert()
VerilogTextReader('NAndGate');

***Verilog modular from NAndGate.v***

// File: NAndGate.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:49:01 2018
```

```
`timescale 1ns/10ps

module NAndGate (
    X0,
    X1,
    Y
);
// NAND Gate demo module
//
// Input:
//   X0(bool): NAnd gate input 0
//   X1(bool): NAnd gate input 1
//
// Output:
//   Y(bool): NAnd gate output

input X0;
input X1;
output Y;
wire Y;

assign Y = (!(X0 && X1));

endmodule
```

▼ 11.5 myHDL to Verilog Testbench

```
In [108]: ▼ #create BitVectora for NAndGate_TBV
X0TVs=intbv(int(''.join(X0TVs.astype(str)), 2))[TestLen:]
X1TVs=intbv(int(''.join(X1TVs.astype(str)), 2))[TestLen:]
X0TVs, bin(X0TVs), X1TVs, bin(X1TVs)
```

```
Out[108]: (intbv(5892), '1011100000100', intbv(3661), '111001001101')
```



```
In [109]: @block
def NAndGate_TBV():
    """
    myHDL -> Verilog testbench for module `NAndGate`
    """
    X0=Signal(bool(0))
    X1=Signal(bool(0))
    Y=Signal(bool(0))

    @always_comb
    def print_data():
        print(X0, X1, Y)

    #Test Signal Bit Vectors
    X0TV=Signal(X0TVs)
    X1TV=Signal(X1TVs)

    DUT=NAndGate(X0, X1, Y)

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TV[i])
            X1.next=int(X1TV[i])
            yield delay(1)

        raise StopSimulation()
    return instances()

TB=NAndGate_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('NAndGate_TBV');
```

```
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from NAndGate_TBV.v***
```

```
// File: NAndGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:49:07 2018
```

```
`timescale 1ns/10ps
```

```
module NAndGate_TBV (
```

```
);
// myHDL -> Verilog testbench for module `NAndGate`
```

```
wire Y;
reg X0 = 0;
reg X1 = 0;
wire [13:0] X0TV;
wire [13:0] X1TV;
```

```

assign X0TV = 14'd5892;
assign X1TV = 14'd3661;

```

```

always @(X1, Y, X0) begin: NANDGATE_TBV_PRINT_DATA
    $write("%h", X0);
    $write(" ");
    $write("%h", X1);
    $write(" ");
    $write("%h", Y);
    $write("\n");
end

```

```

assign Y = (!(X0 && X1));

```

```

initial begin: NANDGATE_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        X0 <= X0TV[i];
        X1 <= X1TV[i];
        # 1;
    end
    $finish;
end

endmodule

```

```

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X0TV
    category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X1TV
    category=ToVerilogWarning

```



Figure 23: NAndGate RTL schematic; Xilinx Vivado 2017.4

 


Figure 24: NAndGate Synthesized Schematic; Xilinx Vivado 2017.4

 


Figure 25: NAndGate Implemented Schematic; Xilinx Vivado 2017.4

▼ 11.6 PYNQ-Z1 Deployment

▼ 11.6.1 Board Circuit

```

In [110]: d=schem.Drawing(unit=.5)
#add elements
G=d.add(l.NAND2,d='right', label='$NAND_2$')


#Gate to led to gnd

d.add(e.LINE, d='right', xy=G.out)
d.add(e.DOT, label='$Y$')
d.add(e.LINE, d='down', l=d.unit*2)
LD0=d.add(e.LED, d='down', label='LD0')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.GND)

d.add(e.LINE, d='left', xy=G.in1, l=d.unit)
d.add(e.DOT, label='$X_0$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='up', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*2)
SW0=d.add(e.SWITCH_SPDT, lftlabel='SW0')
d.add(e.GND, xy=SW0.c)
d.add(e.VDD, xy=SW0.b)

d.add(e.LINE, d='left', xy=G.in2, l=d.unit)
d.add(e.DOT, botlabel='$X_1$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='down', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*4)
SW1=d.add(e.SWITCH_SPDT, lftlabel='SW1')
d.add(e.GND, xy=SW1.c)
d.add(e.VDD, xy=SW1.b)
d.draw()

```

 

▼ 11.6.2 Board Constraint

```
In [111]: ConstraintXDCTextReader('PYNQ_Z1Constraints_NAndGate');

***Constraint file from PYNQ_Z1Constraints_NAndGate.xdc***

## PYNQ-Z1 Board Constraints for NAndGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switchs 0,1
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X0}]
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {X1}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```

▼ 11.6.3 Video of Deployment

NAND Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=Z1rnWfNapas\)](https://www.youtube.com/watch?v=Z1rnWfNapas))


▼ 12 NOR

Definition 9 A NOR Gate is the negated, or the De Morgan equivalent, of an OR Gate. Such that its output will be True if and only if all its inputs are False. Its boolean expression is $Y = \overline{X_0 + X_1}$

One peculiar aspect of the NOR Gate is that from a pure Boolean algebra position it is one of the two "Universal Gates". Which means that any other gate can be constructed from no more than NOR Gates. See

https://en.wikipedia.org/wiki/NOR_logic#Making_other_gates_by_using_NOR_gates (https://en.wikipedia.org/wiki/NOR_logic#Making_other_gates_by_using_NOR_gates) for more info. And while this somewhat holds True for ASIC circuits, this not entirely true in terms of FPGAs
 
```
In [112]: d = schem.Drawing(unit=.5)
G = d.add(l.NOR2, label='$NOR_2$')
d.add(e.DOT_OPEN, xy=G.out, rgtlabel='$Y$')
d.add(e.DOT_OPEN, xy=G.in1, lftlabel='$X_1$')
d.add(e.DOT_OPEN, xy=G.in2, lftlabel='$X_0$')
d.draw()
```



▼ 12.1 Sympy Expression

```
In [113]: X0, X1, Y=symbols('X_0, X_1, Y')
YEq=Eq(Y, Nor(X0,X1)); YEq
```

```
Out[113]: 
$$Y = \neg(X_0 \vee X_1)$$

```

```
In [114]: TruthTabelGenrator(YEq)
```

```
Out[114]:
```

	X_0	X_1	Y
0	0	0	1
1	0	1	0
2	1	0	0
3	1	1	0

```
In [115]: YEqN=lambdify([X0, X1], YEq.rhs, dummify=False)
SystematicVals=np.array(list(itertools.product([0,1], repeat=2)))
SystematicVals, YEqN(SystematicVals[:, 1], SystematicVals[:, 0]).astype(ir
```

```
Out[115]: (array([[0, 0],
                  [0, 1],
                  [1, 0],
                  [1, 1]]), array([1, 0, 0, 0]))
```

▼ 12.2 myHDL Module

```
In [116]: @block
def NOrGate(X0, X1, Y):
    """
    NOr Gate demo module

    Input:
        X0(bool): Or gate input 0
        X1(bool): Or gate input 1

    Output:
        Y(bool): Or gate output

    """
    @always_comb
    def logic():
        #note here that `or` is used since this
        #is a bit wise OR
        Y.next=not(X0 or X1)

        #if `|` had been used the conversion
        #would yield `||` the .all() OR
        # when dealing with bus's and behavior mux's this
        #distiction must be known
        #see:
        # https://stackoverflow.com/questions/17327680/what-is-the-dif

    return instances()
```

▼ 12.3 myHDL Testing

```
In [117]: #generate systmatic and random test values for NOrGate_TB
#stimules inputs X1 and X2
TestLen=10
SystmaticVals=list(itertools.product([0,1], repeat=2))
X0TVs=np.array([i[1] for i in SystmaticVals]).astype(int)
np.random.seed(24)
X0TVs=np.append(X0TVs, np.random.randint(0,2, TestLen)).astype(int)

X1TVs=np.array([i[0] for i in SystmaticVals]).astype(int)
np.random.seed(25)
X1TVs=np.append(X1TVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(X1TVs)
SystmaticVals, X1TVs, X0TVs, TestLen
```

```
Out[117]: ((0, 0), (0, 1), (1, 0), (1, 1)),
array([0, 0, 1, 1, 0, 0, 0, 1, 1, 0, 1, 1, 0, 0]),
array([0, 1, 0, 1, 0, 1, 0, 1, 1, 1, 1, 1, 0, 1, 1]),
14)
```

```

In [118]: Peeker.clear()
X0=Signal(bool(0)); Peeker(X0, 'X0')
X1=Signal(bool(0)); Peeker(X1, 'X1')
Y=Signal(bool(0)); Peeker(Y, 'Y')

DUT=NOrGate(X0, X1, Y)

▼ def NOrGate_TB():
    """
    myHDL only testbench for module `NOrGate`
    """

    @instance
    ▼ def stimules():
        ▼ for i in range(TestLen):
            X0.next=int(X0TVs[i])
            X1.next=int(X1TVs[i])
            yield delay(1)

            raise StopSimulation()

        return instances()

sim=Simulation(DUT, NOrGate_TB(), *Peeker.instances()).run()

```

```

In [119]: Peeker.to_wavedrom('X1', 'X0', 'Y')

```

```

In [120]: NOrData=Peeker.to_dataframe()
NOrData=NOrData[['X1', 'X0', 'Y']]
NOrData

```

```

Out[120]:

```

	X1	X0	Y
0	0	0	1
1	0	1	0
2	1	0	0
3	1	1	0
4	0	0	1
5	0	1	0
6	0	0	1
7	1	1	0
9	0	1	0
10	1	1	0
11	1	0	0
12	0	1	0


```
In [121]: N0rData['YRef']=N0rData.apply(lambda row:YEqN(row['X0'], row['X1']), axis=1)
N0rData
```

```
Out[121]:
```

	X1	X0	Y	YRef
0	0	0	1	1
1	0	1	0	0
2	1	0	0	0
3	1	1	0	0
4	0	0	1	1
5	0	1	0	0
6	0	0	1	1
7	1	1	0	0
9	0	1	0	0
10	1	1	0	0
11	1	0	0	0
12	0	1	0	0

```
In [122]: Test=(N0rData['Y']==N0rData['YRef']).all()
print(f'Module `N0rGate` works as expected: {Test}')
```

Module `N0rGate` works as expected: True

▼ 12.4 Verilog Conversion

```
In [123]: DUT.convert()
          VerilogTextReader('N0rGate');

          ***Verilog modular from N0rGate.v***
```

```
// File: N0rGate.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:49:57 2018
```

```
`timescale 1ns/10ps
```

```
module N0rGate (
    X0,
    X1,
    Y
);
// N0r Gate demo module
//
// Input:
//   X0(bool): Or gate input 0
//   X1(bool): Or gate input 1
//
// Output:
//   Y(bool): Or gate ouput
```

```
input X0;
input X1;
output Y;
wire Y;
```

```
assign Y = (!(X0 || X1));
```

```
endmodule
```

 


Figure 26: N0rGate RTL schematic; Xilinx Vivado 2017.4

 


Figure 27: N0rGate Synthesized Schematic; Xilinx Vivado 2017.4

 


Figure 28: NOrGate Implemented Schematic; Xilinx Vivado 2017.4

▼ 12.5 myHDL to Verilog Testbench

```
In [124]: ▼ #create BitVector for NOrGate_TBV
X0TVs=intbv(int(''.join(X0TVs.astype(str)), 2))[TestLen:]
X1TVs=intbv(int(''.join(X1TVs.astype(str)), 2))[TestLen:]
X0TVs, bin(X0TVs), X1TVs, bin(X1TVs)
```

```
Out[124]: (intbv(5499), '1010101111011', intbv(3180), '110001101100')
```

```
In [125]: @block
def NOrGate_TBV():
    """
    myHDL -> Verilog testbench for module `NOrGate`
    """
    X0=Signal(bool(0))
    X1=Signal(bool(0))
    Y=Signal(bool(0))

    @always_comb
    def print_data():
        print(X0, X1, Y)

    #Test Signal Bit Vectors
    X0TV=Signal(X0TVs)
    X1TV=Signal(X1TVs)

    DUT=NOrGate(X0, X1, Y)

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TV[i])
            X1.next=int(X1TV[i])
            yield delay(1)

        raise StopSimulation()
    return instances()

TB=NOrGate_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('NOrGate_TBV');
```

```
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from NOrGate_TBV.v***
```

```
// File: NOrGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:50:11 2018
```

```
`timescale 1ns/10ps
```

```
module NOrGate_TBV (
```

```
);
// myHDL -> Verilog testbench for module `NOrGate`
```

```
wire Y;
reg X0 = 0;
reg X1 = 0;
wire [13:0] X0TV;
wire [13:0] X1TV;
```

```

assign X0TV = 14'd5499;
assign X1TV = 14'd3180;

always @(X1, Y, X0) begin: NORGATE_TBV_PRINT_DATA
    $write("%h", X0);
    $write(" ");
    $write("%h", X1);
    $write(" ");
    $write("%h", Y);
    $write("\n");
end

assign Y = (!(X0 || X1));

initial begin: NORGATE_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        X0 <= X0TV[i];
        X1 <= X1TV[i];
        # 1;
    end
    $finish;
end

endmodule

```

```

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X0TV
  category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X1TV
  category=ToVerilogWarning

```

▼ 12.6 PYNQ-Z1 Deployment

▼ 12.6.1 Board Circuit

In [126]:


```
d=schem.Drawing(unit=.5)
#add elements
G=d.add(l.NOR2,d='right', label='$NOR_2$')

#Gate to led to gnd

d.add(e.LINE, d='right', xy=G.out)
d.add(e.DOT, label='$Y$')
d.add(e.LINE, d='down', l=d.unit*2)
LD0=d.add(e.LED, d='down', label='LD0')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.GND)

d.add(e.LINE, d='left', xy=G.in1, l=d.unit)
d.add(e.DOT, label='$X_0$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='up', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*2)
SW0=d.add(e.SWITCH_SPDT, lftlabel='SW0')
d.add(e.GND, xy=SW0.c)
d.add(e.VDD, xy=SW0.b)

 d.add(e.LINE, d='left', xy=G.in2, l=d.unit)
d.add(e.DOT, botlabel='$X_1$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='down', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*4)
SW1=d.add(e.SWITCH_SPDT, lftlabel='SW1')
d.add(e.GND, xy=SW1.c)
d.add(e.VDD, xy=SW1.b)
d.draw()
```



▼ 12.6.2 Board Constraint

```
In [127]: ConstraintXDCTextReader('PYNQ_Z1Constraints_N0rGate');

***Constraint file from PYNQ_Z1Constraints_N0rGate.xdc***

## PYNQ-Z1 Board Constraints for NorGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switchs 0,1
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X0}]
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {X1}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```

▼ 12.6.3 Video of Deployment

AND Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=xtFvUx9fSAI\)](https://www.youtube.com/watch?v=xtFvUx9fSAI))

▼ 13 XNOR

Definition 10 An XNOR Gate is the negated, or the De Morgan equivalent, of an XOR Gate. Such that its output will be True if and only if all its inputs are the same. Its boolean expression is typically $Y = X_0 \odot X_1$ using its typical notation, which is a refinement of the \cdot notation used for an AND Gate. But can also be expressed as $Y = X_0 \oplus \overline{X_1}$

```
In [128]: d = schem.Drawing(unit=.5)
G = d.add(1.XNOR2, label='$XNOR_2$')
d.add(e.DOT_OPEN, xy=G.out, rgtlabel='$Y$')
d.add(e.DOT_OPEN, xy=G.in1, lftlabel='$X_1$')
d.add(e.DOT_OPEN, xy=G.in2, lftlabel='$X_0$')
d.draw()
```



▼ 13.1 Sympy Expression

```
In [129]: X0, X1, Y=symbols('X_0, X_1, Y')
#expanded expresion of XNOR
YEq=Eq(Y, X0&X1|~X0&~X1); YEq
```

Out[129]:

$$Y = (X_0 \wedge X_1) \vee (\neg X_0 \wedge \neg X_1)$$

```
In [130]: TruthTabelGenrator(YEq)
```

Out[130]:

	X_0	X_1	Y
0	0	0	1
1	0	1	0
2	1	0	0
3	1	1	1

```
In [131]: YEqN=lambdify([X0, X1], YEq.rhs, dummify=False)
SystematicVals=np.array(list(itertools.product([0,1], repeat=2)))
SystematicVals, YEqN(SystematicVals[:, 1], SystematicVals[:, 0]).astype(ir
```

Out[131]: (array([[0, 0],
[0, 1],
[1, 0],
[1, 1]]), array([1, 0, 0, 1]))

▼ 13.2 myHDL Module

```
In [132]: @block
def XNORGate(X0, X1, Y):
    """
    XNOR Gate demo module

    Input:
    X0(bool): XOR gate input 0
    X1(bool): XOR gate input 1

    Output:
    Y(bool): XOR gate ouput

    """
    @always_comb
    def logic():
        Y.next=not(X0 ^ X1)

    return instances()
```

▼ 13.3 myHDL Testing


```
In [133]: #generate systmatic and random test values for XN0rGate_TB
#stimules inputs X1 and X2
TestLen=10
SystematicVals=list(itertools.product([0,1], repeat=2))
X0TVs=np.array([i[1] for i in SystematicVals]).astype(int)
np.random.seed(26)
X0TVs=np.append(X0TVs, np.random.randint(0,2, TestLen)).astype(int)

X1TVs=np.array([i[0] for i in SystematicVals]).astype(int)
np.random.seed(27)
X1TVs=np.append(X1TVs, np.random.randint(0,2, TestLen)).astype(int)

TestLen=len(X1TVs)
SystematicVals, X1TVs, X0TVs, TestLen
```

```
Out[133]: ((0, 0), (0, 1), (1, 0), (1, 1)),
array([0, 0, 1, 1, 1, 0, 0, 1, 0, 0, 1, 0, 1, 1]),
array([0, 1, 0, 1, 1, 0, 0, 0, 1, 0, 1, 1, 0, 0]),
14)
```

```
In [134]: Peeker.clear()
X0=Signal(bool(0)); Peeker(X0, 'X0')
X1=Signal(bool(0)); Peeker(X1, 'X1')
Y=Signal(bool(0)); Peeker(Y, 'Y')

DUT=XN0rGate(X0, X1, Y)

def XN0rGate_TB():
    """
    myHDL only testbench for module `N0rGate`
    """

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TVs[i])
            X1.next=int(X1TVs[i])
            yield delay(1)

        raise StopSimulation()

    return instances()

sim=Simulation(DUT, XN0rGate_TB(), *Peeker.instances()).run()
```

```
In [135]: Peeker.to_wavedrom('X1', 'X0', 'Y')
```

```
In [136]: XNOrData=Peeker.to_dataframe()
XNOrData=XNOrData[['X1', 'X0', 'Y']]
XNOrData
```

```
Out[136]:
```

	X1	X0	Y
0	0	0	1
1	0	1	0
2	1	0	0
3	1	1	1
5	0	0	1
7	1	0	0
8	0	1	0
9	0	0	1
10	1	1	1
11	0	1	0
12	1	0	0

```
In [137]: XNOrData['YRef']=XNOrData.apply(lambda row:YEqN(row['X0'], row['X1']),
XNOrData
```

```
Out[137]:
```

	X1	X0	Y	YRef
0	0	0	1	1
1	0	1	0	0
2	1	0	0	0
3	1	1	1	1
5	0	0	1	1
7	1	0	0	0
8	0	1	0	0
9	0	0	1	1
10	1	1	1	1
11	0	1	0	0
12	1	0	0	0

```
In [138]: Test=(XNOrData['Y']==XNOrData['YRef']).all()
print(f'Module `XNOrGate` works as expected: {Test}')
```

Module `XNOrGate` works as expected: True

▼ 13.4 Verilog Conversion

```
In [139]: DUT.convert()
VerilogTextReader('XNOrGate');

***Verilog modular from XNOrGate.v***
```

```
// File: XNOrGate.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:50:48 2018
```

```
`timescale 1ns/10ps
```

```
module XNOrGate (
    X0,
    X1,
    Y
);
// XNOR Gate demo module
//
// Input:
//   X0(bool): XOR gate input 0
//   X1(bool): XOR gate input 1
//
// Output:
//   Y(bool): XOR gate output
```


```
input X0;
input X1;
output Y;
wire Y;
```

```
assign Y = (!(X0 ^ X1));
```

```
endmodule
```



Figure 29: XNOrGate RTL schematic; Xilinx Vivado 2017.4

 

Processing math: 100%

Figure 30: XNOrGate Synthesized Schematic; Xilinx Vivado 2017.4

 


Figure 31: XNOrGate Implemented Schematic; Xilinx Vivado 2017.4

▼ 13.5 myHDL to Verilog Testbench

```
In [140]: ▼ #create BitVector for XNOrGate_TBV
X0TVs=intbv(int(''.join(X0TVs.astype(str)), 2))[TestLen:]
X1TVs=intbv(int(''.join(X1TVs.astype(str)), 2))[TestLen:]
X0TVs, bin(X0TVs), X1TVs, bin(X1TVs)
```

```
Out[140]: (intbv(5676), '1011000101100', intbv(3659), '111001001011')
```

```
In [141]: @block
def XNOrGate_TBV():
    """
    myHDL -> Verilog testbench for module `NOrGate`
    """
    X0=Signal(bool(0))
    X1=Signal(bool(0))
    Y=Signal(bool(0))

    @always_comb
    def print_data():
        print(X0, X1, Y)

    #Test Signal Bit Vectors
    X0TV=Signal(X0TVs)
    X1TV=Signal(X1TVs)

    DUT=XNOrGate(X0, X1, Y)

    @instance
    def stimules():
        for i in range(TestLen):
            X0.next=int(X0TV[i])
            X1.next=int(X1TV[i])
            yield delay(1)

        raise StopSimulation()
    return instances()

TB=XNOrGate_TBV()
TB.convert(hdl="Verilog", initial_values=True)
VerilogTextReader('XNOrGate_TBV');
```

```
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
<class 'myhdl._Signal._Signal'> <class '_ast.Name'>
***Verilog modular from XNOrGate_TBV.v***
```

```
// File: XNOrGate_TBV.v
// Generated by MyHDL 0.10
// Date: Mon Sep  3 14:51:02 2018
```

```
`timescale 1ns/10ps
```

```
module XNOrGate_TBV (
```

```
);
// myHDL -> Verilog testbench for module `NOrGate`
```

```
wire Y;
reg X0 = 0;
reg X1 = 0;
wire [13:0] X0TV;
wire [13:0] X1TV;
```

```

assign X0TV = 14'd5676;
assign X1TV = 14'd3659;

always @(X1, Y, X0) begin: XNORGATE_TBV_PRINT_DATA
    $write("%h", X0);
    $write(" ");
    $write("%h", X1);
    $write(" ");
    $write("%h", Y);
    $write("\n");
end

assign Y = (!(X0 ^ X1));

initial begin: XNORGATE_TBV_STIMULES
    integer i;
    for (i=0; i<14; i=i+1) begin
        X0 <= X0TV[i];
        X1 <= X1TV[i];
        # 1;
    end
    $finish;
end

endmodule

```

```

/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X0TV
    category=ToVerilogWarning
/home/iridium/anaconda3/lib/python3.6/site-packages/myhdl/conversion/_t
oVerilog.py:349: ToVerilogWarning: Signal is not driven: X1TV
    category=ToVerilogWarning

```

▼ 13.6 PYNQ-Z1 Deployment

▼ 13.6.1 Board Circuit

In [142]:


```
d=schem.Drawing(unit=.5)
#add elements
G=d.add(l.XNOR2,d='right', label='$XNOR_2$')

#Gate to led to gnd

d.add(e.LINE, d='right', xy=G.out)
d.add(e.DOT, label='$Y$')
d.add(e.LINE, d='down', l=d.unit*2)
LD0=d.add(e.LED, d='down', label='LD0')
d.add(e.LINE, d='down', l=d.unit*2)
d.add(e.GND)

d.add(e.LINE, d='left', xy=G.in1, l=d.unit)
d.add(e.DOT, label='$X_0$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='up', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*2)
SW0=d.add(e.SWITCH_SPDT, lftlabel='SW0')
d.add(e.GND, xy=SW0.c)
d.add(e.VDD, xy=SW0.b)

 d.add(e.LINE, d='left', xy=G.in2, l=d.unit)
d.add(e.DOT, botlabel='$X_1$')
d.add(e.LINE,d='left', l=d.unit)
d.add(e.LINE,d='down', l=d.unit*2)
d.add(e.LINE,d='left', l=d.unit*4)
SW1=d.add(e.SWITCH_SPDT, lftlabel='SW1')
d.add(e.GND, xy=SW1.c)
d.add(e.VDD, xy=SW1.b)
d.draw()
```



▼ 13.6.2 Board Constraint

```
In [143]: ConstraintXDCTextReader('PYNQ_Z1Constraints_XN0rGate');

***Constraint file from PYNQ_Z1Constraints_XN0rGate.xdc***

## PYNQ-Z1 Board Constraints for XN0rGate.v
## Based on https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc (https://github.com/Digilent/digilent-xdc/blob/master/Arty-Master.xdc)

## Switchs 0,1
set_property -dict {PACKAGE_PIN M20 IOSTANDARD LVCMOS33} [get_ports {X0}]
set_property -dict {PACKAGE_PIN M19 IOSTANDARD LVCMOS33} [get_ports {X1}]

##LED 0
set_property -dict {PACKAGE_PIN R14 IOSTANDARD LVCMOS33} [get_ports {Y}]
```

▼ 13.6.3 Video of Deployment

AND Gate myHDL PYNQ-Z1 ([YouTube \(https://www.youtube.com/watch?v=Uys0Zhs7rIU\)](https://www.youtube.com/watch?v=Uys0Zhs7rIU))

```
In [ ]:
```